

Short-Circuited Line

$$\tilde{V}_{sc}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$= -2jV_0^+ \sin \beta z$$

$$\tilde{I}_{sc}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}) = \frac{2V_0^+}{Z_0} \cos \beta z$$

$$Z_{in}^{sc} = \frac{V_{sc}(-l)}{I_{sc}(-l)} = \frac{+2jV_0^+ \sin \beta l}{\frac{2V_0^+}{Z_0} \cos \beta l} = jZ_0 \tan \beta l$$

$$Z_{in}^{sc} = jZ_0 \tan \beta l \quad (m)$$

$$Z_{in} = R_{in} + jX_{in} = jZ_0 \tan \beta l \rightarrow R_{in} = 0$$

$$X_{in} = Z_0 \tan \beta l$$

* If $\beta l > 0 \rightarrow X_{in} = \omega L_{eq} = Z_0 \tan \beta l$

$$\rightarrow L_{eq} = \frac{Z_0 \tan \beta l}{\omega} \rightarrow l = \frac{1}{\beta} \tan^{-1} \frac{\omega L_{eq}}{Z_0}$$

this is the minimum length that results in an equivalent inductance of L_{eq} . Other lengths are $l = n\frac{\lambda}{2} + \frac{1}{\beta} \tan^{-1} \frac{\omega L_{eq}}{Z_0}$

* If $\beta l < 0 \rightarrow \frac{1}{j\omega C_{eq}} = jZ_0 \tan \beta l \rightarrow C_{eq} = -\frac{1}{Z_0 \omega \tan \beta l}$

The minimum length that results in C_{eq} is:

$$Z_0 \tan \beta l = \frac{1}{\omega C_{eq}} \rightarrow \tan \beta l = \frac{1}{Z_0 \omega C_{eq}} \rightarrow \beta l = \pi - \tan^{-1} \left(\frac{1}{Z_0 \omega C_{eq}} \right)$$

because $\tan \beta l \leq 0$

$$\rightarrow l = \frac{1}{\beta} \left(\pi - \tan^{-1} \left(\frac{1}{Z_0 \omega C_{eq}} \right) \right)$$

Of course for all length of $l = n\frac{\lambda}{2} + \frac{1}{\beta} \left(\pi - \tan^{-1} \left(\frac{1}{Z_0 \omega C_{eq}} \right) \right)$ this is valid.


Open Circuit Line

$$Z_L = \infty \rightarrow \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 1 \rightarrow \tilde{V}_{oc}(z) = V_0^+ (e^{-j\beta z} + e^{j\beta z}) = 2V_0^+ \cos \beta z$$

$$\tilde{I}_{oc}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{j\beta z}) = -2j\frac{V_0^+}{Z_0} \sin \beta l$$

$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(0)}{\tilde{I}_{oc}(-l)} \Rightarrow$$

$$Z_{in}^{oc} = -jZ_0 \cot \beta l$$

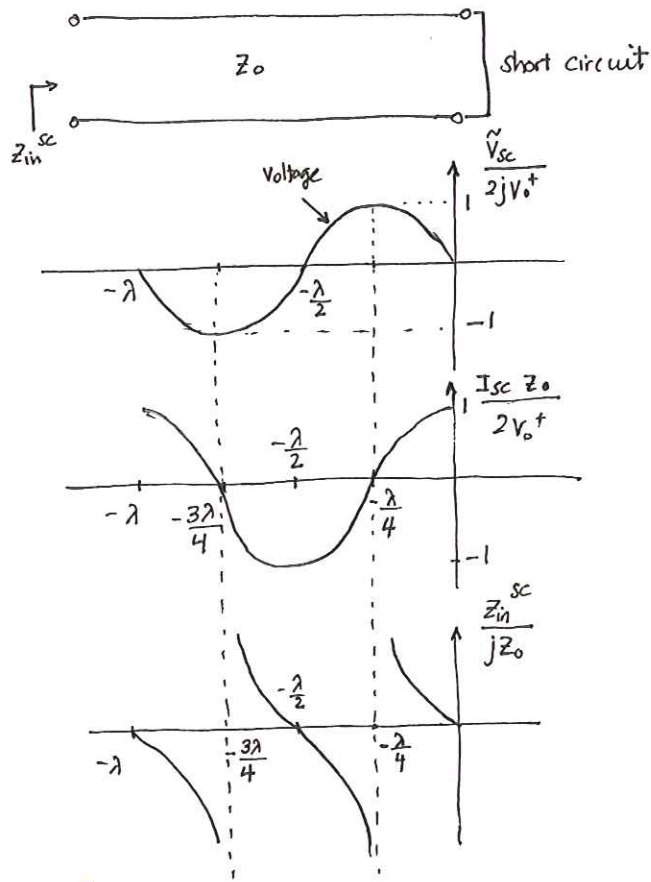

Application of Short-circuit and

Open-circuit Measurement:

Combination of Z_{sc} and Z_{oc} measurement can be used to determine the characteristic impedance of the line Z_0 and its phase constant β :

$$\begin{aligned} Z_{in}^{sc} &= jZ_0 \tan \beta l \\ Z_{in}^{oc} &= -jZ_0 \cot \beta l \end{aligned} \rightarrow \begin{cases} Z_0 = \sqrt{Z_{in}^{sc} Z_{in}^{oc}} \\ \tan \beta l = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}} \end{cases}$$


Example: Read example 2-8 page 67.

Lines of length $l = \frac{n\lambda}{2}$:

$$\text{If } l = \frac{n\lambda}{2} \Rightarrow \beta l = \frac{2\pi}{\lambda} \frac{n\lambda}{2} = n\pi \rightarrow \tan \beta l = \tan n\pi = 0$$

$$\rightarrow Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = Z_L \rightarrow \boxed{Z_{in} = Z_L \text{ for } l = \frac{n\lambda}{2}}$$

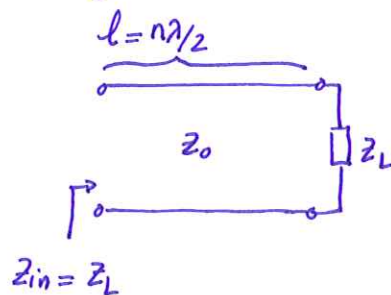In other words, half-wavelength line doesn't modify the load impedance.




Quarter-wave Transformer:

$$\text{Now take } l = \frac{\lambda}{4} + \frac{n\lambda}{2} \rightarrow \tan \beta l = \tan \left(\frac{2\pi}{\lambda} \frac{\lambda}{4} + \frac{2\pi}{\lambda} \frac{n\lambda}{2} \right) = \tan \left(\frac{\pi}{2} + n\pi \right) = \infty$$

$$\rightarrow Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = Z_0 \frac{jZ_0}{jZ_L} = \frac{Z_0^2}{Z_L}$$


$$\boxed{Z_{in} = \frac{Z_0^2}{Z_L} \text{ for } l = \frac{\lambda}{4} + \frac{n\lambda}{2}}$$

Open circuited line:

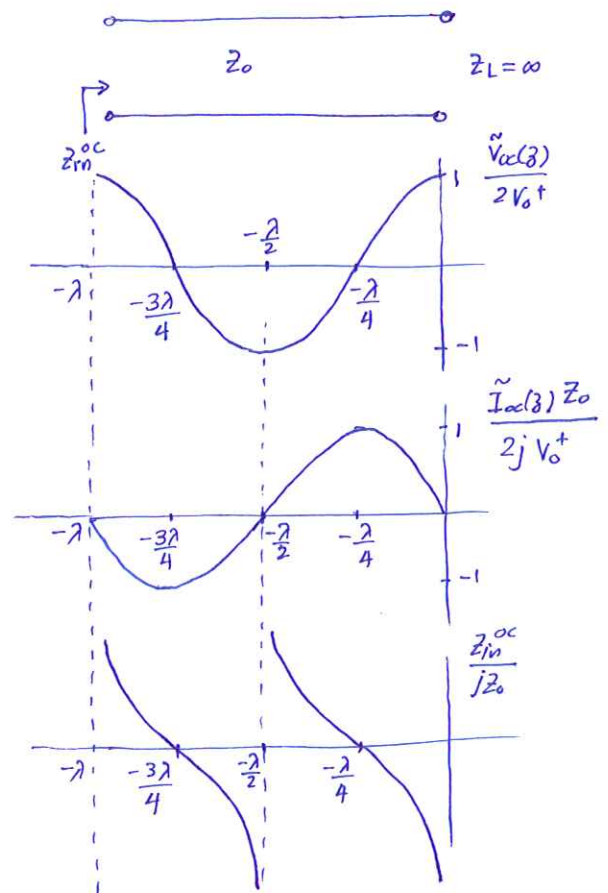

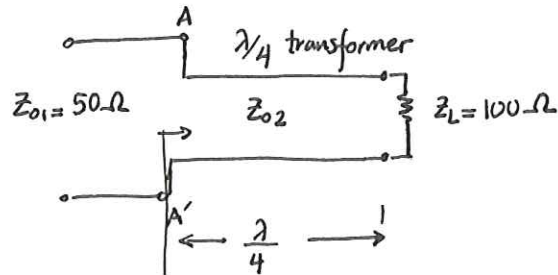Example

we want to match a load impedance of $Z_L = 100\text{-}\Omega$ to a lossless transmission line with $Z_0 = 50\text{-}\Omega$ via a quarter-wave section as shown in the picture. Find the characteristic impedance of the quarter-wave transformer.



$$Z_{in} = \frac{Z_{02}^2}{Z_L} \rightarrow Z_{02} = \sqrt{Z_{in} Z_L} = \sqrt{50 \times 100} = 70.7\text{-}\Omega$$

Matched Transmission Line $Z_L = Z_0$

- for a matched line:
- 1) $Z_L = Z_0 \rightarrow Z_{in} = Z_0$
 - 2) reflectance is zero $\Gamma = 0$
 - 3) all incident power is delivered to the load regardless of l .

Power flow on a lossless transmission line

Instantaneous power: the power carried by the incident wave arrived at the load is equal to:

$$\begin{aligned} P^i(t) &= v^i(t) i^i(t) \\ &= \text{Re}[\tilde{V}^i e^{j\omega t}] \cdot \text{Re}[\tilde{I}^i e^{j\omega t}] \\ &= \text{Re}[|V_0^+| e^{j\phi^+} e^{j\omega t}] \cdot \text{Re}\left[\frac{|V_0^+|}{Z_0} e^{j\phi^+} e^{j\omega t}\right] \\ &= |V_0^+| \cos(\omega t + \phi^+) \cdot \frac{|V_0^+|}{Z_0} \cos(\omega t + \phi^+) \\ &= \frac{|V_0^+|^2}{Z_0} \cos^2(\omega t + \phi^+) \quad \text{instantaneous power incident on the load} \end{aligned}$$

Similarly using $\Gamma = |\Gamma| e^{j\theta_r}$ we can write down the instantaneous power reflected from the load:

$$P^r(t) = v^r(t) \cdot i^r(t) = -|\Gamma|^2 \frac{|V_o^+|^2}{Z_0} \cos^2(\omega t + \phi^+ + \theta_r)$$

Time Average power

We usually want to know the average power flow in the line than the instantaneous power. To calculate the average power P_{av} we can use phasors or the time-domain form. Let's do both:


Time-domain approach:

$$P_{av}^i = \frac{1}{T} \int_0^T P^i(t) dt = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} P^i(t) dt = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} \frac{|V_o^+|^2}{Z_0} \cos^2(\omega t + \phi^+) dt$$

$$P_{av}^i = \frac{|V_o^+|^2}{2Z_0}$$

Similarly for the reflected power:

$$P_{av}^r = -|\Gamma|^2 \frac{|V_o^+|^2}{2Z_0} = -|\Gamma|^2 P_{av}^i$$

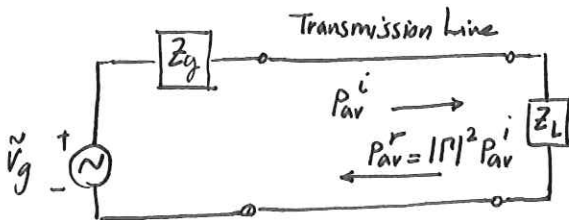

The net power delivered to the load is:

$$P_{av} = P_{av}^i + P_{av}^r = \frac{|V_o^+|^2}{2Z_0} [1 - |\Gamma|^2]$$

Phasor-Domain Approach:

a useful formula for ^{average} power in phasor domain is:


$$P_{av} = \frac{1}{2} \operatorname{Re} [\tilde{V} \cdot \tilde{I}^*]$$

$$P_{av}^i = \frac{1}{2} \operatorname{Re} \left[V_o^+ \cdot \frac{V_o^{+*}}{Z_o} \right] = \frac{|V_o^+|^2}{2Z_o}$$

$$P_{av}^r = \frac{1}{2} \operatorname{Re} \left[\Gamma V_o^+ \cdot \left(-\frac{\Gamma^* V_o^{+*}}{Z_o} \right) \right] = -|\Gamma|^2 \frac{|V_o^+|^2}{2Z_o}$$

Gradient of a Scalar Field:
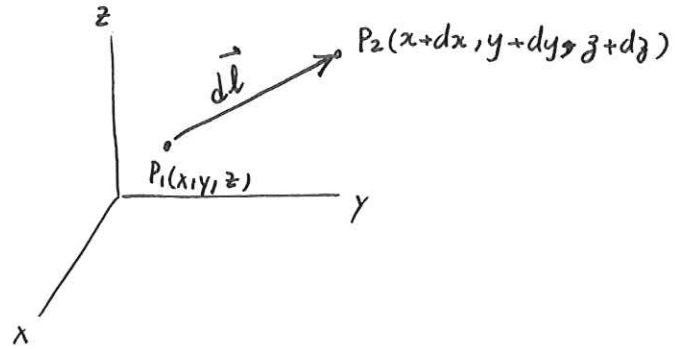
$$\vec{\nabla} T = \text{grad } T \triangleq \frac{\partial T}{\partial x} \hat{x} + \frac{\partial T}{\partial y} \hat{y} + \frac{\partial T}{\partial z} \hat{z}$$



$$dT = \vec{\nabla} T \cdot d\vec{l}$$

del or gradient operator:

$$\nabla \triangleq \hat{x} \frac{\partial}{\partial x} + \hat{y} \frac{\partial}{\partial y} + \hat{z} \frac{\partial}{\partial z} \quad (\text{Cartesian})$$

$$d\vec{l} = \hat{a}_l dl \rightarrow \frac{dT}{dl} = \nabla T \cdot \hat{a}_l$$

In Cylindrical and Spherical Coordinates:

$$\nabla = \hat{r} \frac{\partial}{\partial r} + \hat{\phi} \frac{1}{r} \frac{\partial}{\partial \phi} + \hat{z} \frac{\partial}{\partial z} \quad (\text{cylindrical})$$

$$\nabla = \hat{R} \frac{\partial}{\partial R} + \hat{\theta} \frac{1}{R} \frac{\partial}{\partial \theta} + \hat{\phi} \frac{1}{R \sin \theta} \frac{\partial}{\partial \phi} \quad (\text{spherical})$$

Divergence of a vector Field:

$$\vec{\nabla} \cdot \vec{E} \triangleq \text{div } E = \frac{\partial E_x}{\partial x} + \frac{\partial E_y}{\partial y} + \frac{\partial E_z}{\partial z}$$

For cylindrical & spherical, refer to the back cover of the book.

Divergence Theorem:

$$\int_V \nabla \cdot \vec{E} dv = \oint_S \vec{E} \cdot d\vec{s}$$

Example

Calculate the divergence of each of the following vector fields:

$$a) \vec{E} = \hat{x} 3x^2 + \hat{y} 2y + \hat{z} x^2 z$$

$$b) \vec{E} = \hat{R} \frac{a^3 \cos \theta}{R^2} - \hat{\theta} \left(a^3 \frac{\sin \theta}{R^2} \right)$$

$$\text{Solution: (a)} \quad \vec{\nabla} \cdot \vec{E} = \frac{\partial E_x}{\partial x} + \frac{\partial E_y}{\partial y} + \frac{\partial E_z}{\partial z} = 6x + 0 + x^2 = 6x + x^2$$

$$(b) \quad \vec{\nabla} \cdot \vec{E} = \frac{1}{R^2} \frac{\partial}{\partial R} (R^2 E_R) + \frac{1}{R \sin \theta} \frac{\partial}{\partial \theta} (E_\theta \sin \theta) + \frac{1}{R \sin \theta} \frac{\partial E_\phi}{\partial \phi}$$


$$= \frac{1}{R^2} \frac{\partial}{\partial R} (a^3 \cos \theta) + \frac{1}{R \sin \theta} \frac{\partial}{\partial \theta} \left(- \frac{a^3 \sin \theta}{R^2} \right)$$

$$= 0 - \frac{2a^3 \cos \theta}{R^3} = - \frac{2a^3 \cos \theta}{R^3}$$

Note:

Consider a closed surface in an electric field E :

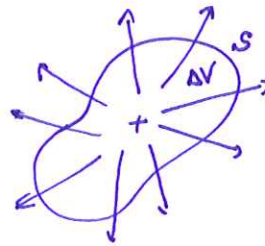□ $\vec{\nabla} \cdot \vec{E}$ is positive if the net flux out of surface S is positive. In other words, if there is a "source" inside the volume encountered by surface S .



□ $\vec{\nabla} \cdot \vec{E}$ is negative if the net flux is inward. In other words if there is a "sink" inside the volume defined by surface S .

□ for a uniform field, the same amount of flux enters volume ΔV as it leaves the volume.

$$\text{So } \vec{\nabla} \cdot \vec{E} = 0$$

We call E here a

"divergenceless" field.

