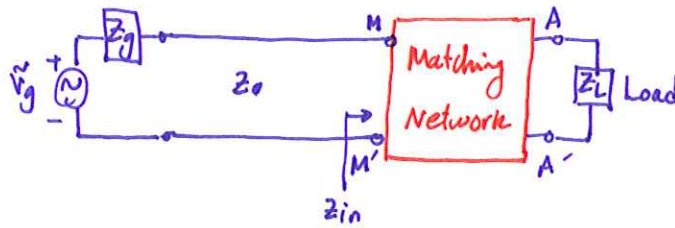


## Impedance Matching

Matched line satisfies  $Z_0 = Z_L \Rightarrow$  no reflection occurs at the load.


Since  $Z_0$  and  $Z_L$  are usually given and cannot be changed in reality, we have to use an alternative way to match the load to the line. We will use an **impedance-matching network** between the load and the line.



If  $Z_{in}$  at  $MM'$  is equal to  $Z_0$ , there is no power reflected to generator.

The matching network usually has no resistance and only consists of capacitors & inductors so there is no ohmic power loss. We may also use a section of transmission line with proper length and termination to make the matching network. This is called **single-stub matching network**.

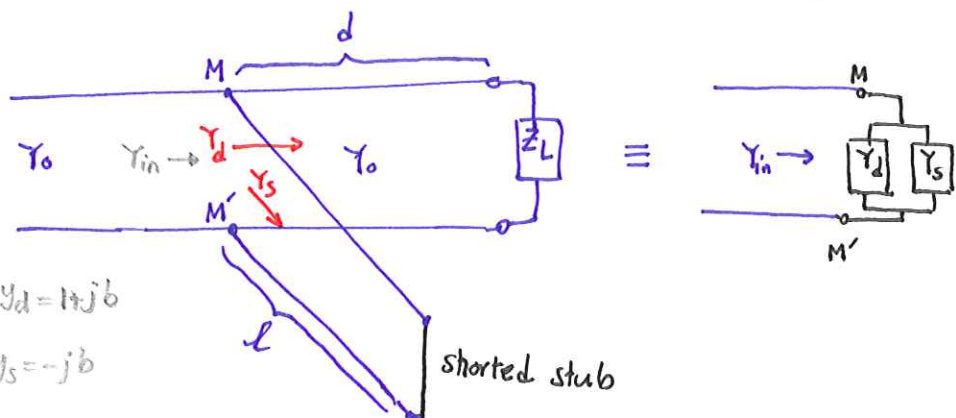If  $Z_L = R_L + jX_L$ , the matching network must convert  $R_L$  to  $Z_0$  and transform the reactive part  $X_L$  to zero. So the matching network has to have at least two degrees of freedom (i.e. two adjustable parameters). For example a **shunt stub** has two adjustable parameters of length ( $l$ ) and distance ( $d$ ) from the load.



Goal:  $Y_d = Y_0 + jB$  or  $y_d = 1 + jb$   
 $Y_s = -jB$  or  $y_s = -jb$

$\Rightarrow Y_{in} = Y_d + Y_s = Y_0$

Since this is shunt stub, it is easier to work with admittance. To match the line we follow the two steps:

- 1) Find  $d$  to transform the load admittance  $Y_L$  to  $Y_d = Y_0 + jB$  at  $MM'$ .
- 2) Find  $l$  of the stub so its input impedance at  $MM'$  is  $Y_s = -jB$

The parallel sum of the two admittances at  $MM'$  is then:


$$Y_{in} = Y_d + Y_s$$

$$= Y_0 + jB - jB = Y_0 \text{ which matched.}$$
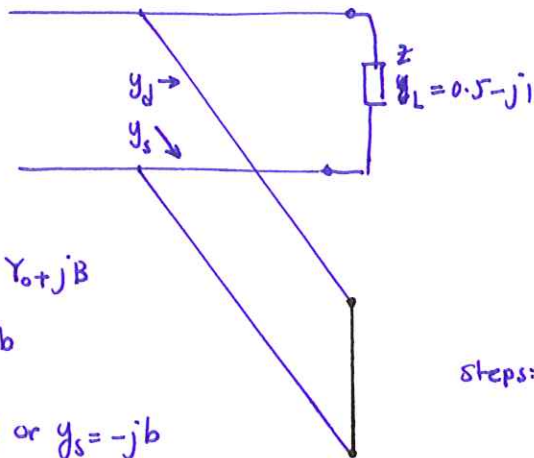
### Example


A  $50\Omega$  line is connected to a load  $Z_L = 25 - j50 (\Omega)$ . Find the position and length of the short-circuited stub to match the line.

Solution:  $Y_L = \frac{Z_L}{Z_0} = 0.5 - j1$



1) We want  $Y_d = Y_0 + jB$   
or  $y_d = 1 + jb$

2) Also  $Y_s = -jB$  or  $y_s = -jb$

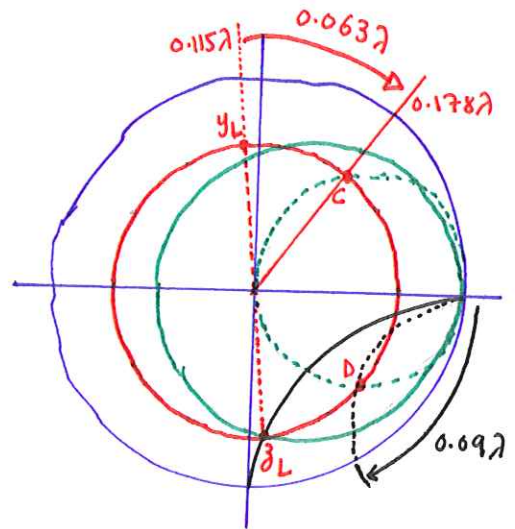

steps: 1) find  $y_L$

- 2) Plot  $S$  circle. when we move away from the load, the admittance moves on this circle
- 3) Plot  $g=1$  circle (this same as  $r=1$  circle) there are usually two crossing points with  $S$  circle. like  $C$  and  $D$  here. So there are also two solutions. let's consider solution for point  $C$ .



4) distance from the load to arrive at  $C$  is:  
 $0.178\lambda - 0.115\lambda = 0.063\lambda$

At this point the load admittance is transformed to  $y_d = 1 + j1.58$

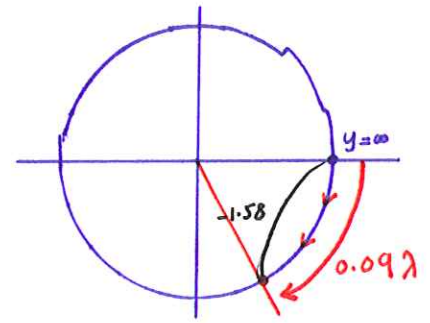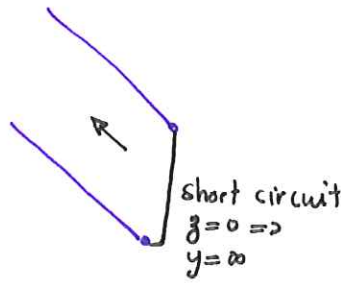5) Find a length of the stub that transforms short circuit ( $y=\infty$ ) to  $y_s = -j1.58$

$y = \infty$  is on the corner of the circle.


Moving from short circuit is like moving towards generator on S circle. here S circle is the smith chart main circle.




Find where the  $b = -j1.58$  circle crosses the S circle.

The length of the stub is from  $y = \infty$  to  $b = -j1.58$ :  $l = 0.34\lambda - 0.25\lambda = 0.09\lambda$

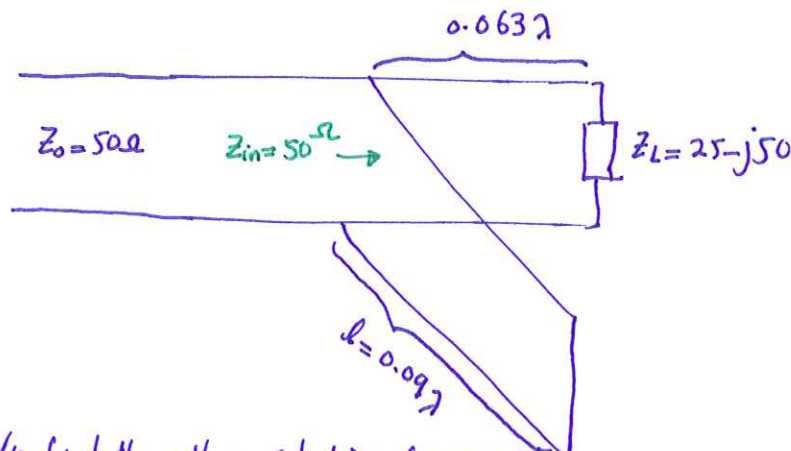\* We could equally look at complex conjugate of C that is D and find the cross-point of the  $b$  circle that passes point D and the smith chart main circle. As shown with dotted black circle on previous chart.



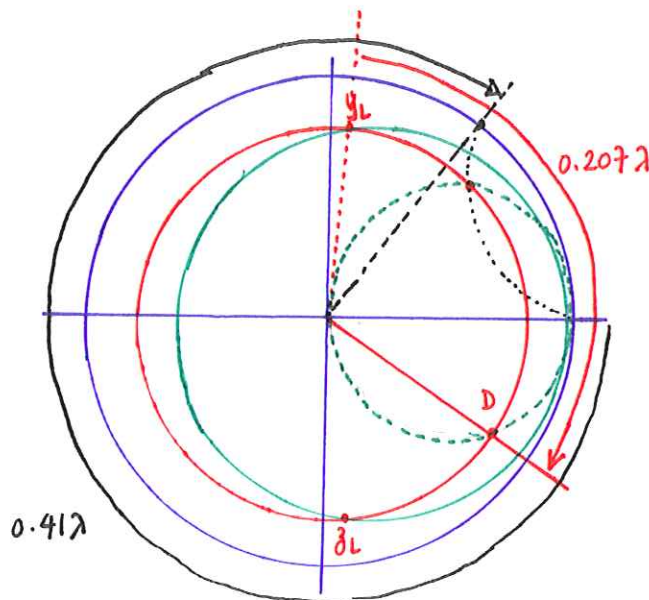We can similarly find the other solution for point D:



$$\begin{cases} d = 0.207\lambda \\ l = 0.41\lambda \end{cases}$$

## Transients on Transmission Lines


So far we have been studying single frequency circuits at steady state. For circuits that the signal is changing with time, we cannot, for example, use Smith chart and we have to study the **transient response** of a voltage (or current) in the line.

### Transient Response


Consider the given circuit:

Assume  $Z_L$  is purely resistive, so all impedances in the circuit are real.

The switch is closed at time  $t=0$ .

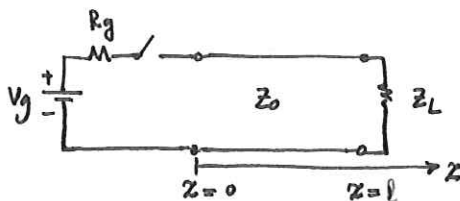

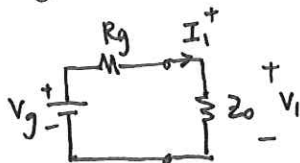At beginning the generator only sees the transmission line impedance  $Z_0$ :



$$\Rightarrow I_1^+ = \frac{V_g}{R_g + Z_0}$$

$$V_1^+ = I_1^+ Z_0 = \frac{V_g Z_0}{R_g + Z_0}$$

$V_1^+$  and  $I_1^+$  constitute a wave that starts to travel in the line with velocity

$u_p = \frac{1}{\sqrt{\mu \epsilon}}$  immediately after the switch is ON. For example if we take  $R_g = 4Z_0$







and  $Z_L = 2Z_0 \rightarrow I_1^+ = \frac{1}{5} V_g$   $V_1^+ = \frac{1}{5} V_g$ . We can now look at  $V$  and  $I$  at different times on the line.

At some time  $t=T$ ,  $V_1^+$  and  $I_1^+$  reach the load and are partly absorbed and partly reflected.

The reflection coefficient is:  $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \stackrel{\text{here}}{=} \frac{2Z_0 - Z_0}{2Z_0 + Z_0} = \frac{1}{3}$ . After the first

reflection, the voltage on the line consists of two voltages:  $V_1^+$  and  $V_1^-$ .

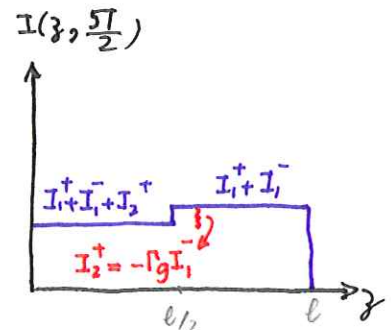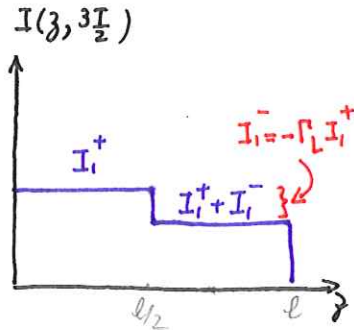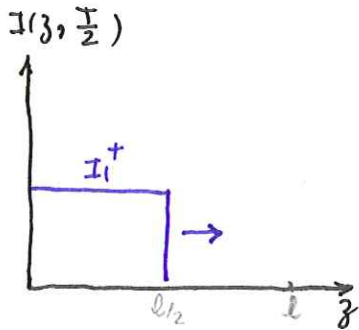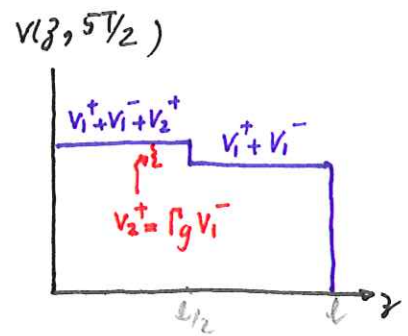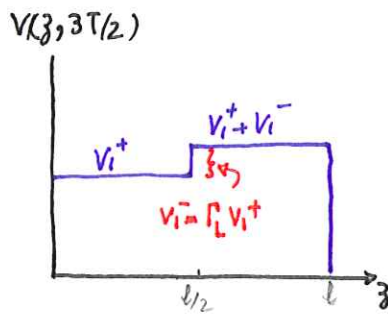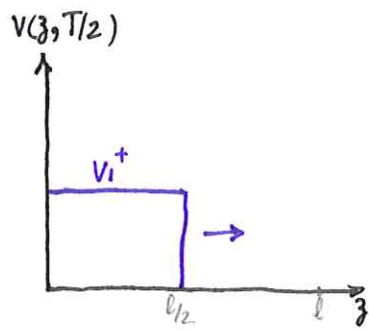At some time  $t=2T$ ,  $V_1^-$  and  $I_1^-$  reach the generator and are again reflected back to the line. They are shown as  $V_2^+$  and  $I_2^+$  in the figure.



$$\Gamma_L = \frac{z_L - z_0}{z_L + z_0} \quad \Gamma_g = \frac{z_g - z_0}{z_g + z_0}$$

So the equilibrium voltage at long time is some of all voltages back and forth:

$$V_\infty = V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + \dots$$

$$= V_1^+ (1 + \Gamma_L + \underbrace{\Gamma_L \Gamma_g + \Gamma_L^2 \Gamma_g^2}_{\Gamma_L^2 \Gamma_g^2} + \underbrace{\Gamma_L^2 \Gamma_g^2 + \Gamma_L^3 \Gamma_g^3}_{\Gamma_L^3 \Gamma_g^3} + \dots)$$

$$= V_1^+ (1 + \Gamma_L + \Gamma_L \Gamma_g (1 + \Gamma_L) + \Gamma_L^2 \Gamma_g^2 (1 + \Gamma_L) + \dots)$$

$$= V_1^+ (1 + \Gamma_L) (1 + \Gamma_L \Gamma_g + \Gamma_L^2 \Gamma_g^2 + \Gamma_L^3 \Gamma_g^3 + \dots)$$

$$= V_1^+ (1 + \Gamma_L) \frac{1}{1 - \Gamma_L \Gamma_g} \rightarrow V_\infty = V_1^+ \frac{1 + \Gamma_L}{1 - \Gamma_L \Gamma_g}$$

if we replace  $\Gamma_L$  &  $\Gamma_g \rightarrow V_\infty = V_1^+ \frac{1 + \frac{z_L - z_0}{z_L + z_0}}{1 - \frac{(z_L - z_0)(z_g - z_0)}{(z_L + z_0)(z_g + z_0)}}$  ;  $V_1^+ = V_g \frac{z_0}{z_g + z_0} \Rightarrow$

$$V_\infty = V_g \frac{z_0 (z_g + z_0 + z_L - z_0)}{z_0^2 + z_L z_g + z_0(z_L + z_g) - z_0^2 - z_L z_g + z_0(z_L + z_g)} = V_g \frac{2z_0 z_L}{2z_0(z_L + z_g)} = V_g \frac{z_L}{z_L + z_g}$$

$$\rightarrow \boxed{V_\infty = V_g \frac{z_L}{z_L + z_g}} \text{ steady state voltage. } \rightarrow I_\infty = \frac{V_\infty}{z_L} = \frac{V_g}{z_g + z_L}$$

This  $V_{oc}$  and  $I_{sc}$  are what we expect as dc response of the circuit: At  $t = \infty$  the voltage variation is not seen anymore and we have a dc circuit.




### Bounce Diagram

The diagram below shows how to

calculate the total voltage (or current)



in a transmission line at location  $z$ , at time  $t$ . As example  $z = \frac{l}{4}$  is

considered in this plot.

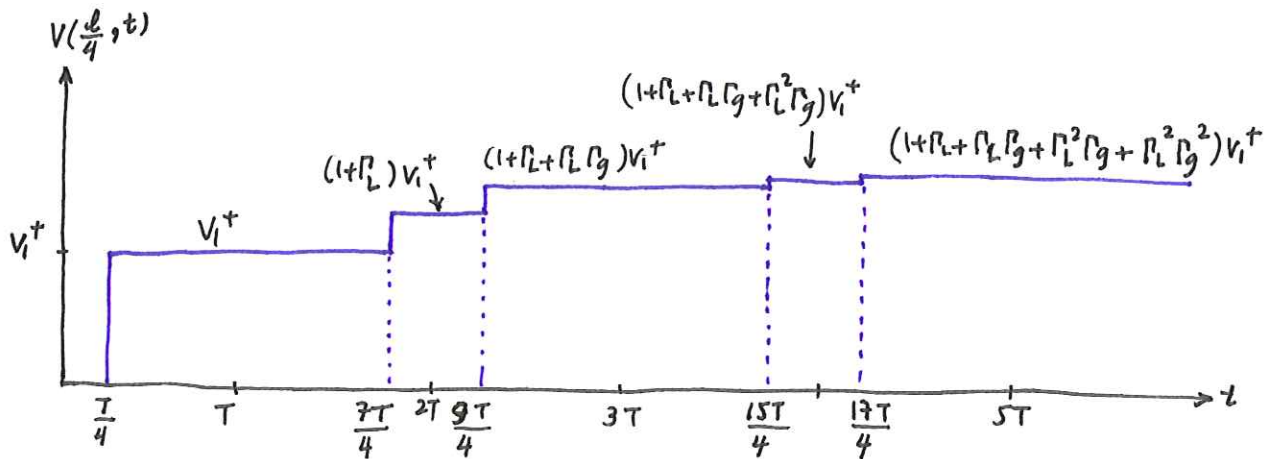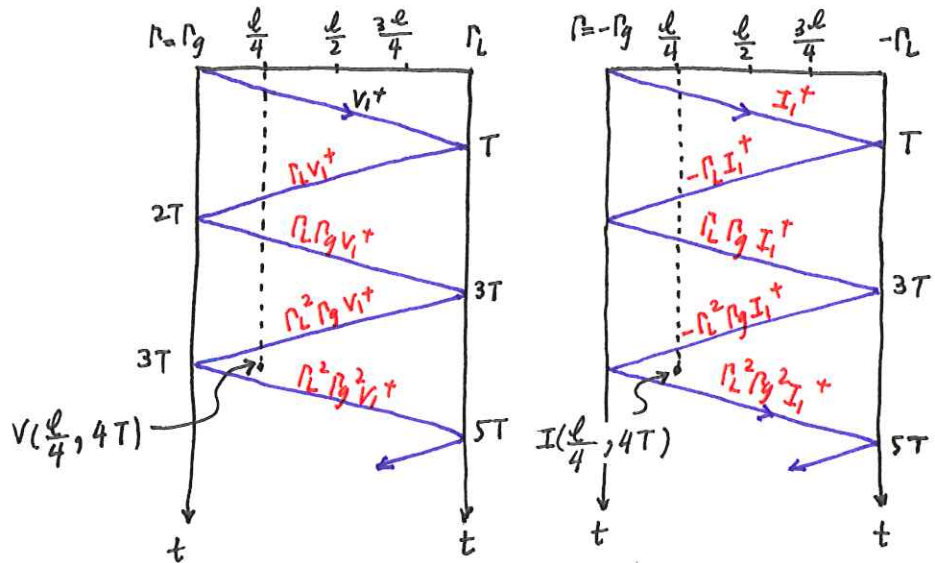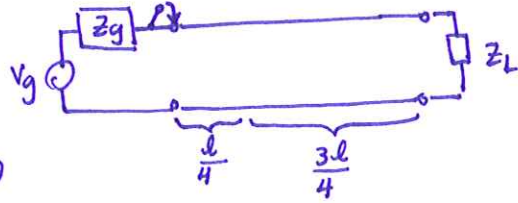
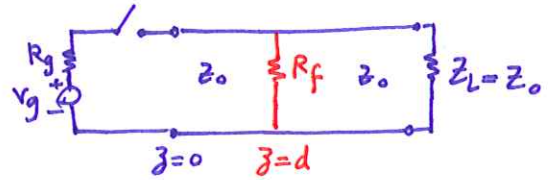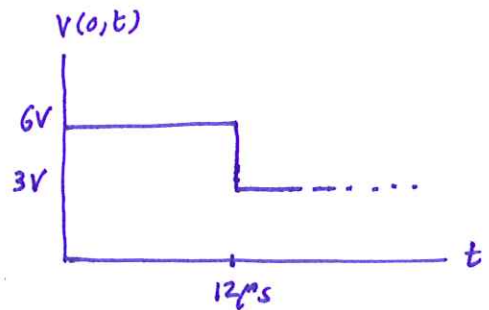
### Example

There is a fault in a matched transmission line. To find the location and strength of the fault, we send a signal into the line and observe the time response of the voltage at the line input. We have observed the voltage shown in the plot.



- Determine the generator voltage
- determine the location of the fault
- find the shunt resistance of the fault.

The line insulating material is teflon with  $\epsilon_r = 2.1$

Solution: Matched line  $\rightarrow R_g = Z_L = Z_0$


$$(a) \quad V_i^+ = \frac{V_g Z_0}{R_g + Z_0} = \frac{V_g Z_0}{2Z_0} = \frac{V_g}{2} \rightarrow V_g = 2V_i^+ = 2 \times 6 = 12 \text{ V}$$

$$(b) \quad u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.1}} = 2.07 \times 10^8 \text{ m/s}$$

the round trip time delay of the echo is:

$$\Delta t = \frac{2d}{u_p} \Rightarrow d = \frac{\Delta t}{2} u_p$$
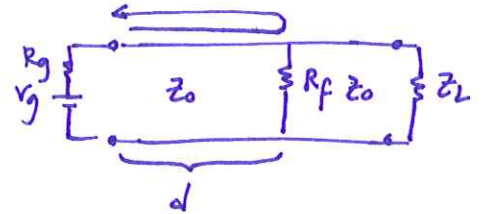
$$d = \frac{12 \times 10^{-6}}{2} \times 2.07 \times 10^8 = 1242 \text{ m}$$



(c) The change in  $V(0,t)$  represent  $V_i^-$ :

$$V_i^- = \Gamma_f V_i^+ = -3 \text{ V} \rightarrow \Gamma_f = -\frac{3}{6} = -\frac{1}{2} = -0.5$$

$$\Gamma_f = \frac{Z_{Lf} - Z_0}{Z_{Lf} + Z_0} \Rightarrow -\frac{1}{2} \rightarrow -2Z_{Lf} + Z_0 = Z_{Lf} + Z_0 \rightarrow Z_{Lf} = \frac{Z_0}{3} = \frac{75}{3} = 25 \Omega$$

$$Z_{Lf} = Z_0 \parallel R_f \rightarrow \frac{1}{Z_{Lf}} = \frac{1}{Z_0} + \frac{1}{R_f} \rightarrow \frac{1}{R_f} = \frac{1}{25} - \frac{1}{75} = \frac{2}{75} \rightarrow R_f = 37.5 \Omega$$