

Problem 2.17

ECEN 3613

$$f = 300 \text{ MHz}$$

lossless

$$Z_0 = 50 \Omega$$

air spaced ( $\mu_r = 1$ ,  $\epsilon_r = 1$ )

$$\text{length} = 2.5 \text{ m}$$

$$Z_L = (40 + j20) \Omega$$

$$Z_{in}(l) = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

$$v_p = f\lambda = \frac{\omega}{\beta}$$

$$c = \frac{\omega}{\beta} \Rightarrow \beta = \frac{2\pi f}{c} = \frac{2\pi(3 \times 10^8)}{3 \times 10^8} = 2\pi \Rightarrow \beta l = 2\pi \left(\frac{5}{2}\right) = 5\pi$$

hard way:

$$Z_{in}(2.5) = 50 \left[ \frac{40 + j20 + j50 \tan(5\pi)}{50 + j(40 + j20) \tan(5\pi)} \right] \quad \tan(5\pi) = \tan(\pi) = 0$$

$$Z_{in}(2.5) = 50 \left[ \frac{40 + j20}{50} \right]$$

$$Z_{in}(2.5) = \boxed{40 + j20}$$

easy way:

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{3 \times 10^8} = 1 \text{ m} \Rightarrow \frac{\lambda}{2} = \frac{1}{2} \text{ m} \Rightarrow l = 5 \left(\frac{\lambda}{2}\right)$$

$$Z_{in}\left(\frac{\lambda}{2}\right) \text{ repeats every } \frac{\lambda}{2} \therefore Z_{in}\left(-\frac{\lambda}{2}\right) = Z_L = \boxed{40 + j20}$$


Problem Q.18 ECEN 3613

Lossless

$$l = 0.35\lambda$$

$$Z_0 = 100\Omega$$

$$Z_L = (60 + j30)\Omega$$

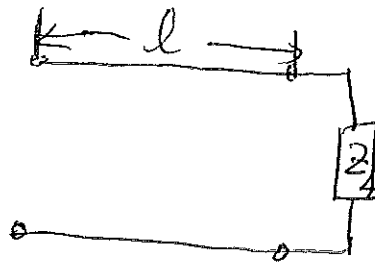

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{60 + j30 - 100}{60 + j30 + 100} = \frac{-40 + j30}{160 + j30} = \frac{50 \angle 143.13^\circ}{162.98 \angle 10.62^\circ}$$

$$\Gamma = 0.3071 \angle 132.51^\circ \quad (\text{or } -0.2075 + j0.2264)$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.3071}{1 - 0.3071} = \frac{1.3071}{0.6929}$$

$$S = 1.886$$

$$\beta = \frac{2\pi}{\lambda} \quad l = 0.35\lambda \Rightarrow \beta l = 2\pi(0.35) = 126^\circ$$

$$Z_{in}(-l) = Z_0 \left[ \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right] = 100 \left[ \frac{60 + j30 + j100 \tan(126^\circ)}{100 + j(60 + j30) \tan(126^\circ)} \right]$$

$$= 100 \left[ \frac{60 - j107.64}{141.29 - j82.58} \right] = 100 \frac{123.23 \angle -60.86^\circ}{163.65 \angle -30.31^\circ}$$

$$= 75.30 \angle -30.55^\circ$$

$$Z_{in}(-l) = 64.75 - j38.27\Omega$$

Problem 2.19 ECEN 3613

lossless

$Z_L = 0$  (short circuit)

$$l = \frac{\lambda}{4}$$

$$Z_{in}(-l) = Z_0 \left[ \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)} \right]$$

$$\beta = \frac{2\pi}{\lambda} \quad l = \frac{\lambda}{4} \Rightarrow \beta l = \frac{\pi}{2} \quad \tan \frac{\pi}{2} = \infty$$

$$\Rightarrow Z_{in}\left(-\frac{\lambda}{4}\right) = Z_0 \left[ \frac{\frac{Z_L}{\infty} + j Z_0}{\frac{Z_0}{\infty} + j Z_L} \right] = \frac{Z_0^2}{Z_L}$$

$$Z_{in}^{sc}\left(-\frac{\lambda}{4}\right) = \frac{Z_0^2}{Z_L}$$

$$\text{But } Z_L = 0 \Rightarrow Z_{in}^{sc} = \frac{Z_0^2}{0} = \infty$$

$$\therefore Z_{in}^{sc}\left(-\frac{\lambda}{4}\right) = \text{open circuit}$$

# Problem 2.22 EEEN 3613

$$l = 6 \text{ m}$$

$$W = 8\pi \times 10^7 \text{ (} f = 40 \text{ MHz)}$$

$$Z_0 = 150 \Omega$$

$$V_g = 5 \angle -30^\circ \text{ (cos ref)}$$


loss loss

$$V_g(t) = 5 \cos(8\pi \times 10^7 t - 30^\circ) \text{ V}$$

$$Z_g = 150 \Omega$$

$$\epsilon_r = 2.25$$

$$Z_L = 150 - j150 \Omega$$

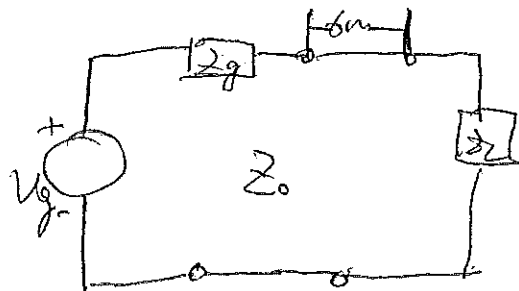

$$(a) \lambda_p = \lambda f = \frac{W}{\beta} \quad V_p = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\epsilon_r \mu_0 \epsilon_0}} = \frac{c}{\sqrt{\epsilon_r}}$$

$$\lambda = \frac{c}{f \sqrt{\epsilon_r}} = \frac{3 \times 10^8}{10^8 \times 1.5} = 2 \text{ m}$$

$$\boxed{\lambda = 5 \text{ m}}$$

$$\Rightarrow \beta = \frac{W}{V_p} = \frac{2\pi}{\lambda} = \frac{2\pi}{5}$$

$$(b) \Gamma_{\text{load}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - j150 - 150}{150 - j150 + 150} = \frac{-j150}{300 - j150} = \frac{50 \angle -90^\circ}{300 \angle -26.6^\circ} = 0.164 \angle -63.4^\circ$$

$$= 0.164 \angle -63.4^\circ$$

$$\boxed{\Gamma = 0.164 \angle -63.4^\circ}$$

$$(c) Z_{in}(-l) = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

$$Z_{in}(-6) = 150 \left[ \frac{150 - j150 + j150 \tan 1.65}{150 + j(150 - j150) \tan 1.65} \right] = 150 \frac{438.13 \angle 69.98^\circ}{552.9 \angle 56.65^\circ} = 118.91 \angle 13.33^\circ$$

$$Z_{in}(-6) = \boxed{115.71 + j27.42 \Omega}$$

$$(d) \tilde{V}_i = \frac{Z_{in}}{Z_g + Z_{in}} \tilde{V}_g = \left( \frac{115.71 \angle 13.33^\circ}{150 + 115.71 + j27.42} \right) (5 \angle -30^\circ) = \frac{584.55 \angle -16.67^\circ}{267.12 \angle 5.89^\circ}$$

$$= 2.226 \angle -22.56^\circ$$

$$\boxed{V_i = 2.226 \angle -22.56^\circ \text{ V}}$$

$$(e) v_i(t) = 2.226 \cos(8\pi \times 10^7 t - 22.56^\circ) \text{ V}$$

Problem 2.25 ECEN 3613

lossless

$Z_L$  is short circuit ( $Z_L = 0$ )

desire open circuit at input


line repeats every  $\frac{\lambda}{2}$ , "inverts" every  $\frac{\lambda}{4}$

so a quarter wave line (or odd multiples of  $\frac{\lambda}{4}$ ) would appear as open.

i.e.,  $l = \frac{\lambda}{4} + n\frac{\lambda}{2}$ ,  $n = 0, 1, 2, \dots$

or  $l = n\frac{\lambda}{4}$ ,  $n$  odd

Problem 2.27 ECE 3613

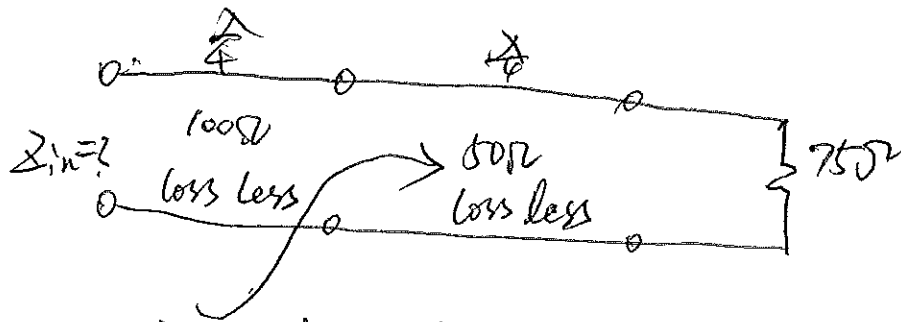

$Z_{in\text{mid}}$  will be the load for the  $100 \Omega$  section

$$\beta = \frac{2\pi}{\lambda} \Rightarrow \beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \quad \text{so } \tan \beta l = \infty \quad \therefore Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_{in\text{mid}} = \frac{(50)^2}{75} = \boxed{33.33 \Omega}$$

$$Z_{in} = \frac{(100)^2}{Z_{in\text{mid}}} = \frac{(100)^2}{33.33} = 300$$


$$Z_{in} = \boxed{300 \Omega}$$

Problem 2.27 ECEM 3613

$$f = 100 \text{ MHz } (1 \times 10^8 \text{ Hz})$$

300  $\Omega$  line (assumed lossless)

$$Z_L = 73 \Omega \text{ (antenna)}$$

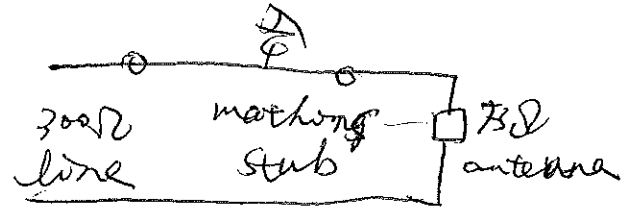

$$(a) Z_{in \text{ stub}} = Z_0^2 \frac{Z_L}{Z_0}, \text{ length} = \frac{\lambda}{4}$$

$$\text{We want } Z_{in \text{ stub}} = 300 \Omega \Rightarrow Z_0 \text{ stub} = \sqrt{(300)(73)} = \boxed{148 \Omega}$$

(b) Two-wire,  $d = 2.5 \text{ cm}$   $\epsilon_r = 2.6$

$$v_p = f\lambda = \frac{c}{\sqrt{\epsilon_r}} \quad \lambda = \frac{c}{\sqrt{\epsilon_r} f} = \frac{3 \times 10^8}{\sqrt{2.6} \times 10^8} = \frac{3}{\sqrt{2.6}} = 1.8665 \text{ m}$$

$$\frac{\lambda}{4} = \boxed{0.4665 \text{ m}}$$

Ref Table 2.2 P55:

Two wire, lossless ( $R' = 0$   $G' = 0$ )  $a$  = wire radius

$$Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln \left[ \frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1} \right] \quad d = \dots \text{ separation}$$

$$\text{let } g = \frac{d}{2a} \quad f = Z_0 \sqrt{\epsilon_r} / 120$$

$$\Rightarrow f = \ln [g + \sqrt{g^2 - 1}] \quad g + \sqrt{g^2 - 1} = e^f \quad \sqrt{g^2 - 1} = e^f - g$$

$$g^2 - 1 = e^{2f} - 2e^f g + g^2 \Rightarrow g = \frac{e^{2f} + 1}{2e^f}$$

$$\text{then } \frac{d}{2a} = \frac{e^{\frac{2 \times 0.4665}{0.4665}} + 1}{2e^{\frac{0.4665}{0.4665}}} = \frac{54.377}{14.612}$$

$$\frac{d}{2a} = 3.7214 \Rightarrow \boxed{a = 3.36 \text{ mm}}$$

$\tilde{V}_g = 300V$


lossless line

$Z_g = 50\Omega$

$W/Z_0 = 50S$

$Z_L = 75\Omega$

$d = 0.15\lambda$

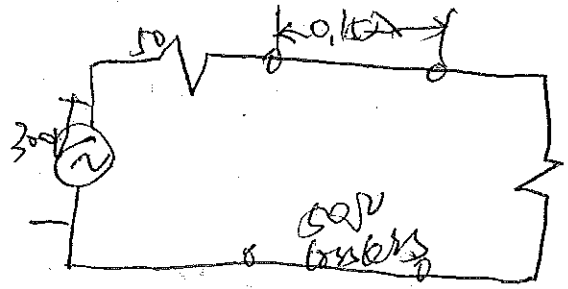

Note: matched at source  
( $\Gamma_{source} = 0$ )

(a)  $Z_{in}(-d) = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} \right)$

$\beta = \frac{2\pi}{\lambda}, \beta d = \frac{2\pi}{\lambda} \times 0.15 = 0.3\pi (54^\circ)$

$Z_{in}(-d) = 50 \left( \frac{75 + j50 \tan 54^\circ}{50 + j75 \tan 54^\circ} \right) = 50 \left( \frac{1.5 + j1.376k}{1 + j2.064k} \right)$

$= 50 \frac{2.0758 \angle 42.5^\circ}{2.294 \angle 69.15^\circ}$

$Z_{in}(-d) = 44.37 \angle -21.62^\circ = \boxed{41.25 - j16.35 \Omega}$

(b)  $\tilde{V}_i = \frac{Z_{in}}{Z_{in} + Z_g} \tilde{V}_g = \frac{44.37 \angle -21.62^\circ}{41.25 - j16.35 + 50} (300)$

$= \frac{13311 \angle -21.62^\circ}{92.70 \angle -10.16^\circ} = \boxed{143.6 \angle -11.46^\circ V}$

$\tilde{I}_i = \frac{\tilde{V}_i}{Z_{in}} = \frac{143.6 \angle -11.46^\circ}{44.37 \angle -21.62^\circ} = \boxed{3.236 \angle 10.16^\circ}$

(c)  $P_{in} = \frac{1}{2} \text{Re} [\tilde{V}_i \tilde{I}_i^*] = \frac{1}{2} \text{Re} [(143.6 \angle -11.46^\circ) (3.236 \angle -10.16^\circ)^*]$

$= \frac{1}{2} \text{Re} [464.7 \angle -21.62^\circ] = \frac{1}{2} (464.7) \cos(-21.62^\circ) = \boxed{216W}$

(d)  $\tilde{V}_L = \tilde{V}_g \Gamma_{L=0} = V_0^+ (1 + \Gamma), \tilde{I}_L = \tilde{I} \Gamma_{L=0} = \frac{V_0^+}{Z_0} (1 - \Gamma)$


$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{75 - 50}{75 + 50} = \frac{25}{125} = \frac{1}{5}, V_0^+ = \frac{Z_{in}}{Z_g + Z_{in}} \tilde{V}_g = \frac{1}{\frac{Z_g}{Z_{in}} + 1} \tilde{V}_g$

$V_0^+ = 143.6 \angle -11.46^\circ \left( \frac{1}{(1 + \frac{1}{5}) \cos 54^\circ + j(1 - \frac{1}{5}) \sin 54^\circ} \right)$

$V_0^+ = \frac{143.6 \angle -11.46^\circ}{0.9573 \angle 42.54^\circ} = 150 \angle -54^\circ \Rightarrow \tilde{V}_L = (1 + \frac{1}{5}) 150 \angle -54^\circ$   
 $\tilde{V}_L = 180 \angle -54^\circ$



Problem 2.33 ECEN 3613

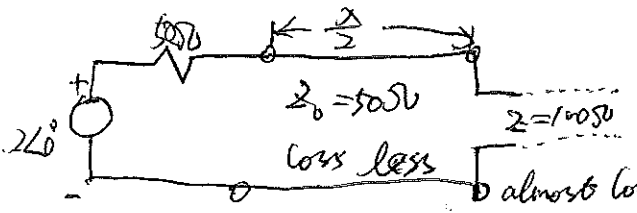

infinitely long ( $l \gg \lambda$ ) so that at end  $e^{-\alpha l} \approx 0!$   
 i.e., no reflections because no voltage to reflect!

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi \text{ (or } 180^\circ)$$

so  $\tan \beta l = 0$       $e^{j\pi} = -1, e^{-j\pi} = -1$

$$\Gamma = \frac{100 - 50}{100 + 50} = \frac{50}{150} = \frac{1}{3}, \quad Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] = 50 \left[ \frac{100}{50} \right] = 100$$

$$V_o^+ = \left( \frac{Z_{in}}{Z_g + Z_{in}} \right) V_g \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right) = \left( \frac{100}{50 + 100} \right) 2 \angle 0^\circ \left( \frac{1}{-1 + \frac{1}{3}(-1)} \right) = -1 = 1 \angle 180^\circ$$

$$V_i = \frac{Z_{in}}{Z_g + Z_{in}} V_g = \frac{100}{50 + 100} 2 \angle 0^\circ = \frac{4}{3} \angle 0^\circ \quad I_i = \frac{V_i}{Z_{in}} = \frac{4}{300} \angle 0^\circ$$

$$P_i = \frac{1}{2} \text{Re} [V_i I_i^*] = \frac{1}{2} \text{Re} \left[ \frac{4}{3} \angle 0^\circ \frac{4}{300} \angle 0^\circ \right] = \frac{8}{400} \text{ W} = 8.8 \text{ mW} \left[ \frac{80}{9} \text{ mW} \right]$$

$$P_w^i = \frac{|V_o^+|^2}{2Z_0} = \frac{1}{2(50)} = \frac{1}{100} \text{ W} = 100 \text{ mW} \left[ \frac{90}{9} \text{ mW} \right]$$

$$P_w^r = -|\Gamma|^2 P_w^i = -\left(\frac{1}{3}\right)^2 100 \text{ mW} = -\frac{10}{9} \text{ mW}$$

$$P_w^t = P_i$$

$P_i$  goes to the load as well (lossless line)

Power check:

incident:	$\frac{90}{9} \text{ mW}$
reflected:	$-\frac{10}{9} \text{ mW}$
delivered:	$\frac{80}{9} \text{ mW}$

checks  $\frac{90}{9} - \frac{10}{9} = \frac{80}{9}!$

Problem 3.33 ECEN 3613

$$\vec{\nabla} T = e^{-2z} \hat{a}_z, \quad T = 10 \text{ at } z = 0$$

$$\vec{\nabla} T = \frac{\partial T}{\partial z} \hat{a}_z = \frac{dT}{dz} \hat{a}_z \text{ [Cartesian or Cylindrical]}$$

because only one variable

$$\frac{dT}{dz} = e^{-2z}$$

$$dT = e^{-2z} dz$$

$$\int dT = \int e^{-2z} dz$$

$$T = \frac{e^{-2z}}{-2} + k \text{ (k is the constant of integration)}$$

$$\text{at } z=0, \quad T=10$$

$$\Rightarrow 10 = -\frac{1}{2} + k \Rightarrow k = 10.5$$

$$T(z) = 10.5 - 0.5 e^{-2z}$$

<Text answer is for  $\vec{\nabla} T = e^{3z} \hat{a}_z$ >

Problem 3.38 ECEN 3613

(a)  $\vec{E}$  points along  $\hat{a}_R \Rightarrow \vec{E} = E_R \hat{a}_R$

(b)  $|\vec{E}|$  is a function of  $R$  only  $\Rightarrow |\vec{E}| = E_R = E_R(R)$   
 a function of  $R$ , not times  $R$ !

(c)  $\vec{E}|_{\text{origin}} = 0 \Rightarrow E_R(R)|_{R=0} = 0$

(d)  $\nabla \cdot \vec{E} = 12$  everywhere  $\Rightarrow \frac{1}{R^2} \frac{d}{dR} (R^2 E_R) = 12 \Rightarrow \frac{d}{dR} (R^2 E_R) = 12R^2$

$$d(R^2 E_R) = 12R^2 dR$$

$$R^2 E_R(R) = 4R^3 + R$$

for  $R=0$ ,  $E_R(0) \cdot R^n = 0 \Rightarrow R=0$

$$R^2 E_R(R) = 4R^3$$

$$E_R(R) = 4R$$

$$\vec{E} = 4R \hat{a}_R$$