

Q-37

$$Z_L = 100 \Omega$$

$$S = 2.5$$


$$Z_0 = ?$$

$$Z_L = \frac{Z_L}{Z_0} \Rightarrow Z_0 = \frac{Z_L}{Z_L}$$

$$\rightarrow Z_0 = \frac{100}{0.4} = 250 \Omega$$

or

$$Z_0 = \frac{100}{2.5} = 40 \Omega$$

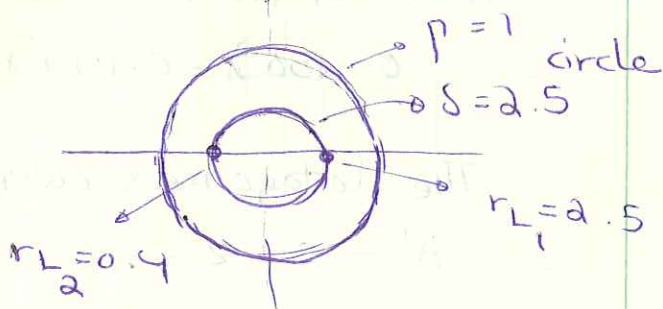Q-38

$$Z_0 = 50 \Omega \text{ lossless line}$$

$$\text{load } Z_L = 50 + j50 \Omega$$

$$\rightarrow Z_L = 1 + 0.5j \text{ (A)}$$

$$|\Gamma| = \frac{18.5 \text{ mm}}{78 \text{ mm}} = 0.237$$

$$\theta_r = 76.3^\circ \text{ (B)} \rightarrow \Gamma = 0.23 e^{j76.3}$$

$$S = 1.62 \text{ (A')}$$

$$\text{at B} \rightarrow 0.144 \lambda \xrightarrow{\text{thus}} 0.35 \lambda \text{ toward the generator} \rightarrow \begin{matrix} 0.144 \lambda \\ 0.35 \lambda \\ \hline 0.494 \lambda \end{matrix} \text{ (C)}$$

$$\text{at (A'')} \quad z_{in} = 0.61 - j0.02$$

$$Z_{in} = Z_0 \times z_{in} \Rightarrow Z_{in} = 30.5 - j1.0 \Omega$$

for y_{in} opposite point from z_{in} on S circle at A''

$$\rightarrow Y_{in} = 1.62 + j0.07$$

$$Y_{in} = \frac{y_{in}}{Z_0} = 32.4 + j1.40 \times 10^{-3} \text{ per}$$

p.2
continued
→

To travel from A to A' one must travel

$$0.250\lambda - 0.144\lambda = 0.106\lambda \rightarrow \text{the shortest line length}$$

The voltage max occurs at

$$A' \rightarrow z = -0.106\lambda$$

$$= 0.106\lambda$$

2.39

lossless line 50Ω

(a) For short circuit $z_L = 0 + j0$ (A) at 0.00λ

Since a lossless line repeats every $\lambda/2$

$\Rightarrow 2.3\lambda$ towards generator
equivalent to

0.3λ toward the generator

↓
(B)

where $z_{in} = 0 - j3.07$

$$\Rightarrow Z_{in} = z_{in} \times Z_0$$

$$= -j154\Omega$$

(b) $Y_{in} = -j0.04 \Rightarrow Y_{in} = -j2$ (c)

\downarrow
 $Y_{in} = Y_{in} Z_0$

\rightarrow D for z_{in}

\downarrow

$$\overline{AD} = 0.074\lambda + n\frac{\lambda}{2}$$

$$n = 0, 1, 2, \dots$$

2-41

lossless line

$l = \frac{\lambda}{8}$

length = $\frac{3\lambda}{8}$

$Z_{in} = -j2.5 \Omega \rightarrow z_{in} = -j0.025 (A)$

$Z_L = ?$

at 0.496λ

and is 0.375λ

toward the load

$\Rightarrow 0.496\lambda$

-0.375λ

0.121λ

Here:

(a) $Z_L = 0 + j0.95 \quad \leftarrow (B)$

$\rightarrow Z_L = j95 \Omega$

(b) open circuit line therefore

at $Z_L = \infty (C) \Rightarrow$

, which is at

0.250λ

an open circuit line

with $Z_{in} = j0.025$

must have a length

of 0.250λ

-0.004λ

0.246λ

2-42

lossless line 75Ω

length = 0.6λ

$S = 1.8 \rightarrow S$ circle must pass through $S = 1.8$

$\theta_r = -60^\circ$

$|\Gamma| = Z_L, Z_{in} = ?$

Circle of this radius

$|\Gamma| = \frac{S-1}{S+1} = \frac{0.8}{2.8} = 0.285 (A)$

p.4

Intersection of circle of $|r|$ and the line of constant θ_r is at the load, Z_L , which has a value $Z_L = 1.15 - j0.63$ at 0.3335λ

$$\rightarrow Z_L = Z_L Z_0 = 86.25 - j47.25 \Omega$$

\downarrow
75 Ω

0.6 λ toward the generator \equiv equiv. 0.1λ

$$\rightarrow 0.3335\lambda + 0.1\lambda = 0.4335\lambda \text{ at (C)}$$

where $Z_{in} = 0.64 - j0.29$

$$\Rightarrow Z_{in} = 48 - j21.75 \Omega$$

$$\frac{2-45}{-}$$

50 Ω lossline

0.6 $\lambda \equiv 0.1\lambda$ equivalent

$$Z_L = 50 + j25 \Omega \rightarrow Z_L = 1 + j0.5 \text{ (A)}$$

$$\text{at } 0.3\lambda \rightarrow R = 30 \Omega$$

$$Z_{in} = ? \quad \left\{ \begin{array}{l} \text{at } Z'_L = 30 \Omega \\ Z'_L = 0.6 \end{array} \right.$$

Need to get Y_{inL} due to Z_L parallel it with Y'_L due to Z'_L

$$\text{get net } Y'_{in} = Y_{inL} + Y'_L$$

$$Z'_L = \frac{30 \Omega}{50} = 0.6$$

$$Y'_L = 1.67$$

corresponding normalized load admittance at 0.394λ

$$\frac{0.1445\lambda + 0.3\lambda}{-}$$

$$0.4445\lambda$$

A \rightarrow B for 0.3λ
 Z_{inL} at (C)

Z_{inL} to Y_{inL} at (D)

$$Y_{inL} = 1.37 + j0.46$$

$$+ \quad 1.67$$

$$Y'_{in} = 3.04 + j0.46$$

at (E)

$$\rightarrow Z_{inF} = 0.283 - j0.048$$

Now go to CW 0.3λ

to get Z_{in} (overall)

$$0.4915\lambda$$

$$+ 0.3\lambda$$

$$0.7915\lambda$$

$$- 0.5$$

$$0.2915\lambda \text{ at G}$$

then at H

$$Z_{in} = 1.95 - j1.38$$

$$Z_{in} = 97.5 - j69 \Omega$$

$$\underline{2.46}$$

50 Ω lossless line

$$Z_L = 75 - j20 \Rightarrow z_L = 1.5 - j0.4 \text{ (A)}$$

y_L at (B)

$$0.0425\lambda \rightarrow 0.145\lambda$$

$$- 0.0425\lambda$$

$$0.1025\lambda$$

$$\text{at (C): } y_{in} = 1 + j0.52$$

$$\hookrightarrow \text{at (E) } -j0.52$$

$$\Rightarrow \text{Length} = 0.4238\lambda$$

$$0.25\lambda$$

$$0.1738\lambda$$

p.6

d-50

lossless line $l = 1\text{m}$

$Z_0 = 50\ \Omega$

$v_p = \frac{2}{3}c$ $Z_L = 25\ \Omega \Rightarrow v_p = 2 \times 10^8\ \text{m/sec}$

$V_g = 60\ \text{V}$ $R_g = 100\ \Omega$ for 1m , $T = \frac{l}{v_p} = \frac{1}{2 \times 10^8} = 5\ \text{nsec}$



$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{25}{75} = -\frac{1}{3}$

$\Gamma_G = \frac{Z_G - Z_0}{Z_G + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = +\frac{1}{3}$

$25\ \text{nsec} = 5T$

$V_1^+ = \frac{Z_0}{Z_0 + Z_G} V_g = \frac{50}{150} 60$

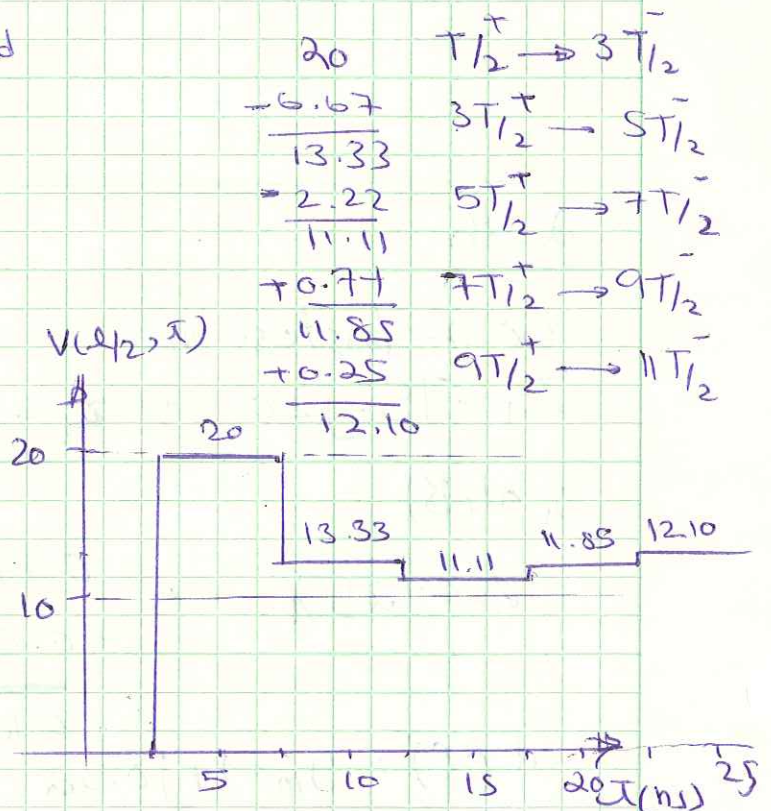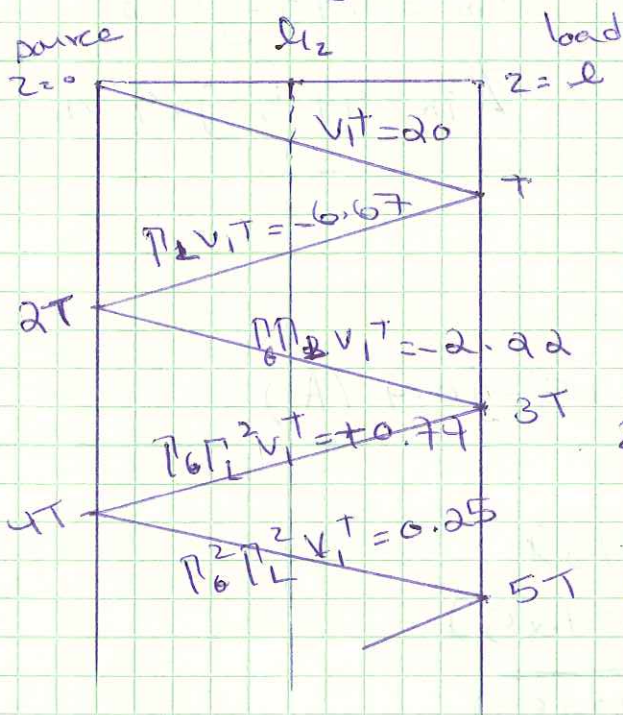$\Rightarrow V_1^+ = \frac{1}{3} (60) = 20$




Q-53

$$Z_0 = 50 \Omega$$

$$Z_L = 0$$

$$\epsilon_r = 4$$

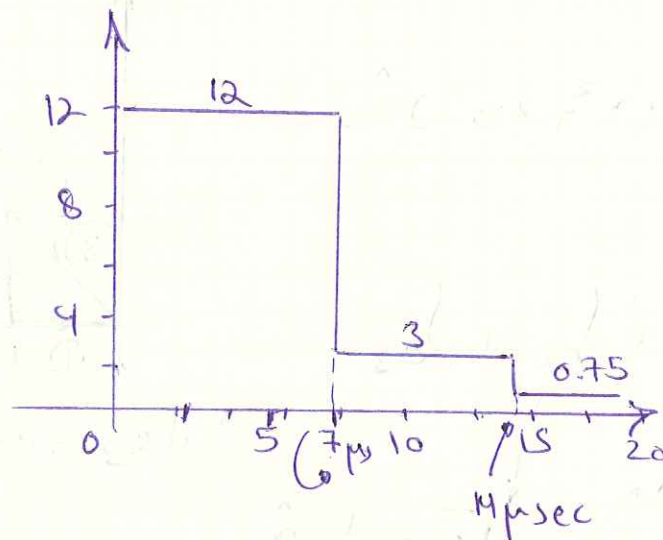

$$\frac{Z_0}{v_p} = 7 \mu s$$

$$\rightarrow v_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{2} = 1.5 \times 10^8$$

$$d = \frac{(7 \times 10^{-6})(1.5 \times 10^6)}{2} = 525 \text{ m}$$

$$V_1^+ = 12 = \frac{Z_0}{R_g + Z_0} V_g$$

$$\Gamma_L \Gamma_G V_1^+ = 3$$

$$\Gamma_L^2 \Gamma_G V_1^+ = 0.75 \quad \rightarrow \Gamma_L \Gamma_G = \frac{3}{12} = \frac{1}{4}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - 50}{0 + 50} = -1 \Rightarrow \Gamma_G = -\frac{1}{4}$$


$$\Gamma_G = \frac{R_g - 50}{R_g + 50} = -\frac{1}{4} \Rightarrow 5R_g = 150 \rightarrow R_g = 30$$

$$12 = \left(\frac{50}{30 + 50} \right) V_g \Rightarrow V_g = 19.2 \text{ V}$$

p. 8

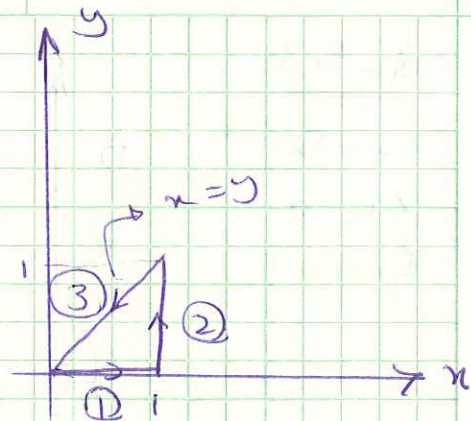3.43

$$\vec{E} = xy \hat{a}_x - (x^2 + 2y^2) \hat{a}_y$$



(a) $\oint \vec{E} \cdot d\vec{e} = ?$

$$\oint \vec{E} \cdot d\vec{e} = \int_{c_1} + \int_{c_2} + \int_{c_3}$$

$$d\vec{e}_1 = dx \hat{a}_x \quad y=0$$

$$d\vec{e}_2 = dy \hat{a}_y \quad x=1$$

$$d\vec{e}_3 = dx \hat{a}_x + dy \hat{a}_y$$

$$\rightarrow \int_{c_1} = \int_0^1 [(xy \hat{a}_x - (x^2 + 2y^2) \hat{a}_y) \cdot dx \hat{a}_x]_{y=0} = 0$$

$$\int_{c_2} = \int_0^1 [(xy \hat{a}_x - (x^2 + 2y^2) \hat{a}_y) \cdot dy \hat{a}_y]_{x=1} = \int_0^1 -(1 + 2y^2) dy = -5/3$$

$$\int_{c_3} = \int_0^1 [xy \hat{a}_x - (x^2 + 2y^2) \hat{a}_y] \cdot (dx \hat{a}_x + dy \hat{a}_y) = \int_0^1 xy dx - \int_0^1 (x^2 + 2y^2) dy \Big|_{x=y} = +2/3$$

$$\rightarrow \oint \vec{E} \cdot d\vec{e} = -5/3 + 0 + 2/3 = -1$$

(b) $\int_S (\nabla \times \vec{E}) \cdot d\vec{s} = \oint \vec{E} \cdot d\vec{e}$ Stokes Theorem


$$d\vec{s} = dx dy \hat{a}_z$$

$$\nabla \times \vec{E} = \begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \partial/\partial x & \partial/\partial y & \partial/\partial z \\ E_x & E_y & E_z \end{vmatrix} = -3x \hat{a}_z$$

$$\rightarrow \int (\nabla \times \vec{E}) \cdot d\vec{s} = -3 \int_0^1 \int_0^1 x dx dy = -1$$

3-45
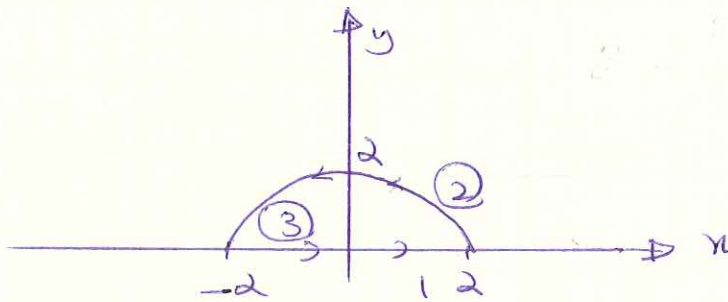
$$\vec{B} = r \cos \varphi \hat{a}_r + 2 \sin \varphi \hat{a}_\varphi$$



$$(a) \int_C \vec{B} \cdot d\vec{e} = ?$$

$$\left\{ \begin{array}{l} d\vec{e}_1 = dr \hat{a}_r \quad \varphi = 0 \quad z = 0 \quad , r |_0^2 \\ d\vec{e}_2 = 2 d\varphi \hat{a}_\varphi \quad , z = 0 \quad , \varphi |_0^\pi \\ d\vec{e}_3 = dr \hat{a}_r \quad \varphi = \pi \quad , z = 0 \quad , r |_{-2}^0 \end{array} \right.$$

$$\rightarrow \vec{B} \cdot d\vec{e}_1 = r \cos \varphi dr \Big|_{\varphi=0}$$

$$\rightarrow \int_0^2 r \cos \varphi dr = 2$$

$$\vec{B} \cdot d\vec{e}_2 = 2 \sin \varphi d\varphi \rightarrow \int_0^\pi = -2 \cos \varphi \Big|_0^\pi = 4$$

$$\vec{B} \cdot d\vec{e}_3 = r \cos \varphi dr \Big|_{\varphi=\pi} \rightarrow \int_{-2}^0 = \frac{-r^2}{2} \Big|_{-2}^0 = 2$$

$$\rightarrow \oint_C = 8$$

$$(b) \int_S (\nabla \times \vec{B}) \cdot d\vec{a}$$

$$\nabla \times \vec{B} = \left(\frac{1}{r} \frac{\partial B_z}{\partial \varphi} - \frac{\partial B_\varphi}{\partial z} \right) \hat{a}_r + \left(\frac{\partial B_r}{\partial z} - \frac{\partial B_z}{\partial r} \right) \hat{a}_\varphi + \frac{1}{r} \left(\frac{\partial r B_r}{\partial r} - \frac{\partial B_r}{\partial \varphi} \right) \hat{a}_z$$

p. 10

$$\rightarrow = \frac{1}{r} (\sin \varphi + r \sin \varphi) \hat{a}_z$$

$$\vec{ds} = r dr d\varphi \hat{a}_z \quad r|_0^2 \quad \varphi|_0^{2\pi}$$

$$\rightarrow \int = -4 \cos \varphi \Big|_0^{2\pi} = 8$$

B-49

(a) $V = 4\pi y^2 z^3 \rightarrow \nabla^2 V = 4(0 + 2xz^3 + 6xy^2z)$

(b) $V = x^2 + y^2 + z^2 \rightarrow \nabla^2 V = 0$

(c) $V = \frac{3}{x^2 + y^2} \rightarrow \nabla^2 V = \frac{12}{(x^2 + y^2)^2}$

$$\begin{aligned} \hookrightarrow \text{or } V = \frac{3}{r^2} &\rightarrow \nabla^2 V = \frac{1}{r} \frac{\partial}{\partial r} \left(r \frac{\partial V}{\partial r} \right) \\ &= \frac{12}{(r^2)^2} \end{aligned}$$

(d) $V = 5e^{-r} \cos \varphi$


$$\begin{aligned} \hookrightarrow \nabla^2 V &= \frac{1}{r} \frac{\partial}{\partial r} \left(r \frac{\partial V}{\partial r} \right) + \frac{1}{r^2} \frac{\partial^2 V}{\partial \varphi^2} + \frac{\partial^2 V}{\partial z^2} \\ &= 5e^{-r} \cos \varphi \left(1 - \frac{1}{r} - \frac{1}{r^2} \right) \end{aligned}$$

(e) $V = 10e^{-R} \sin \theta$


$$\begin{aligned} \hookrightarrow \nabla^2 V &= \frac{1}{R^2} \frac{\partial}{\partial R} \left(R^2 \frac{\partial V}{\partial R} \right) + \frac{1}{R^2 \sin \theta} \frac{\partial}{\partial \theta} \left(\sin \theta \frac{\partial V}{\partial \theta} \right) \\ &\quad + \frac{1}{R^2 \sin^2 \theta} \frac{\partial^2 V}{\partial \varphi^2} \\ &= 10e^{-R} \left[\left(1 - \frac{2}{R} \right) \sin \theta + \frac{\cos^2 \theta - \sin^2 \theta}{R^2 \sin \theta} \right] \end{aligned}$$

2-37

The Smith Chart


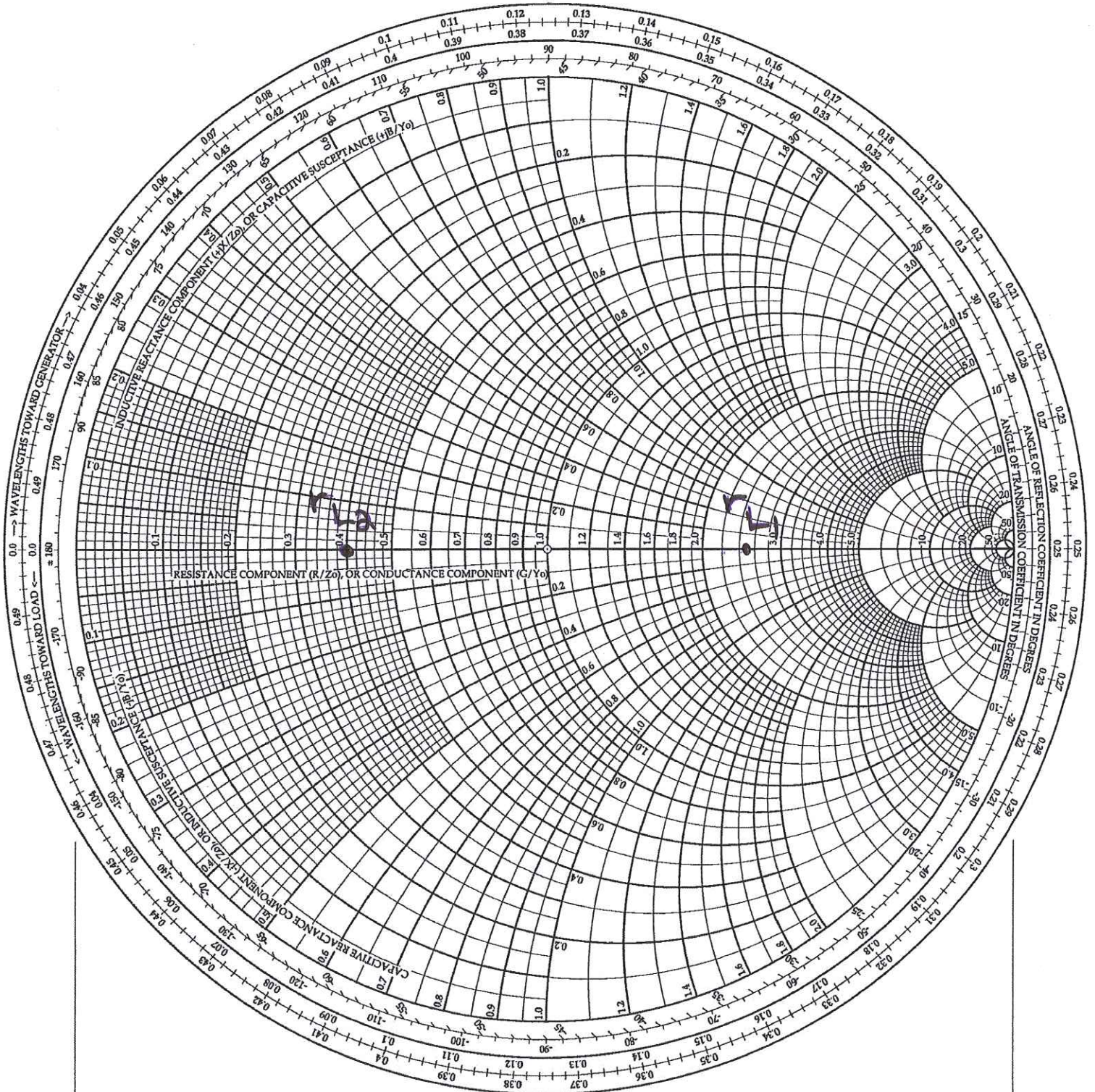


RADIALLY SCALED PARAMETERS

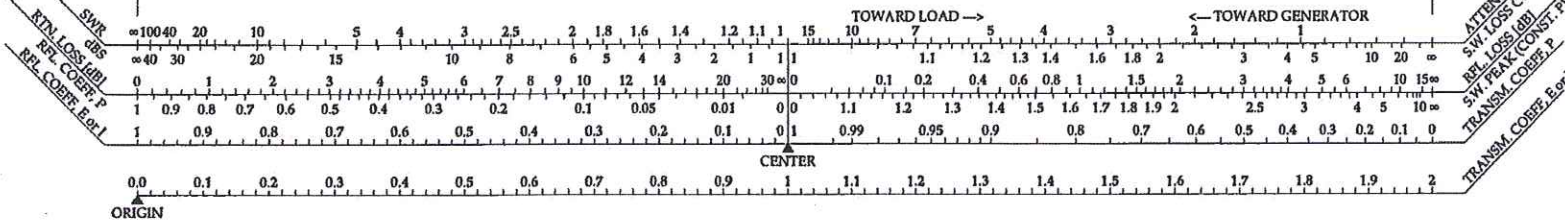


2-38

The Smith Chart

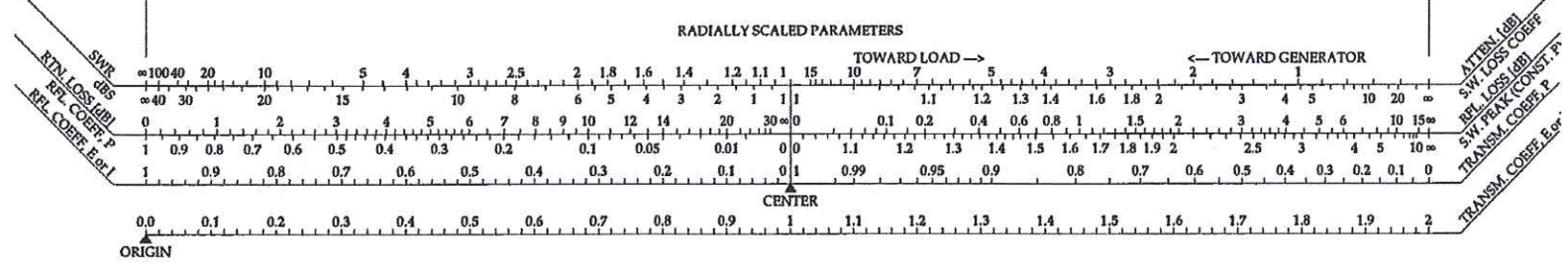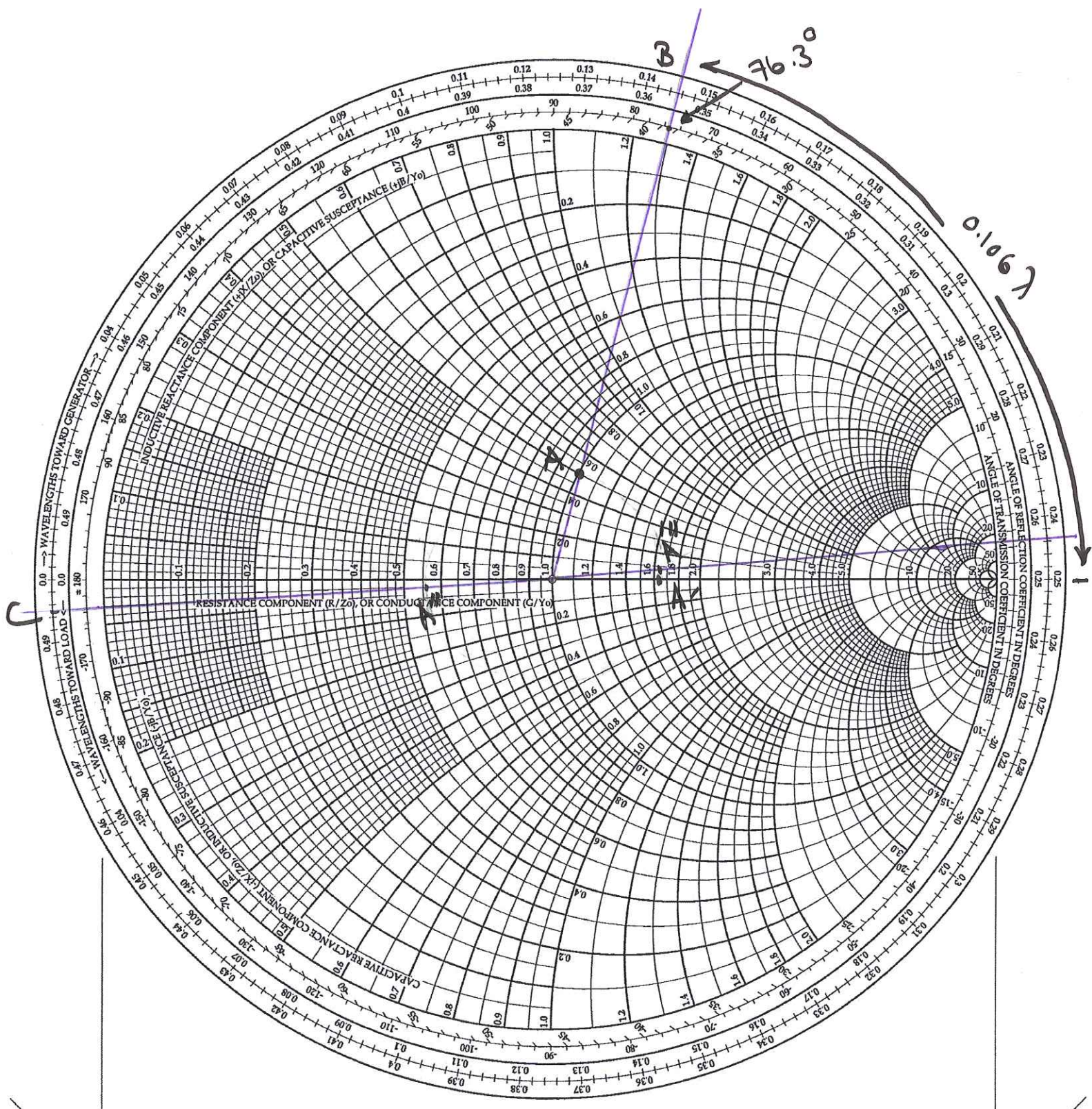


2-39

The Smith Chart

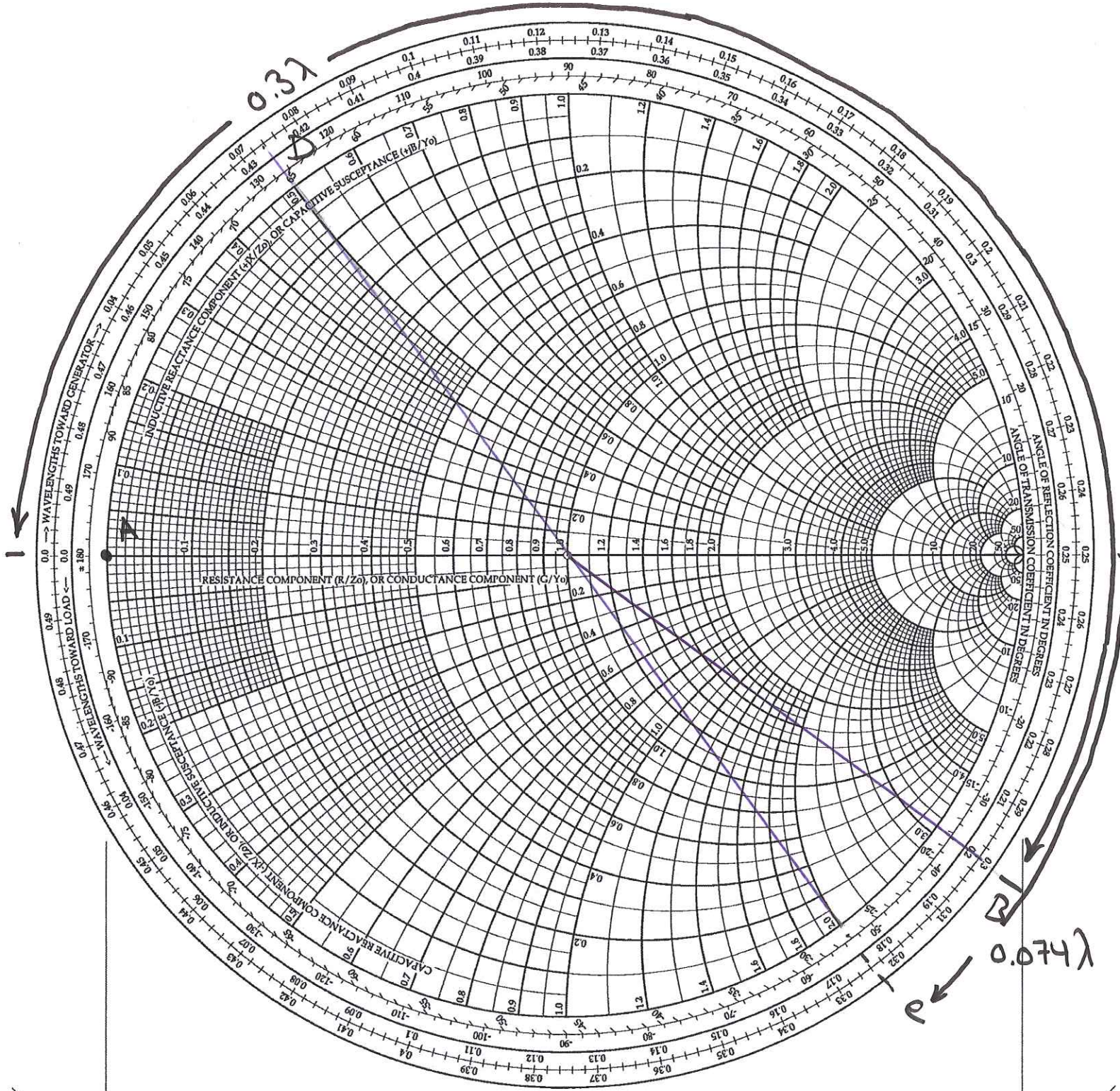


RESISTANCE COMPONENT (R/Z_0), OR CONDUCTANCE COMPONENT (G/Y_0)

RADIALLY SCALED PARAMETERS

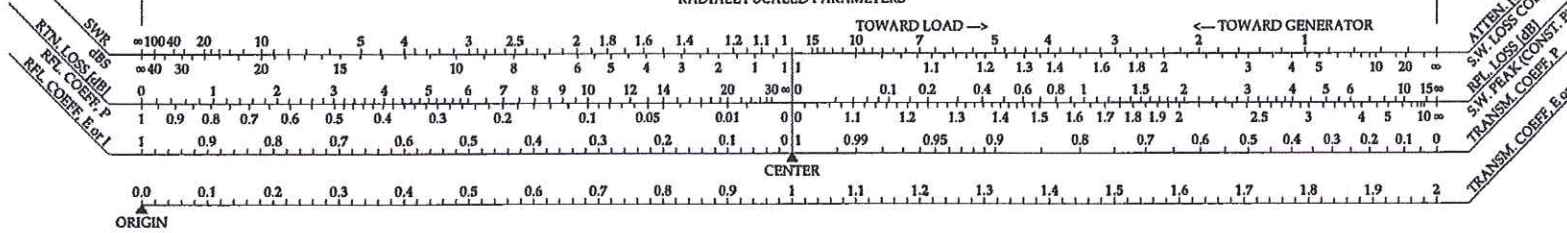


2-41

The Smith Chart

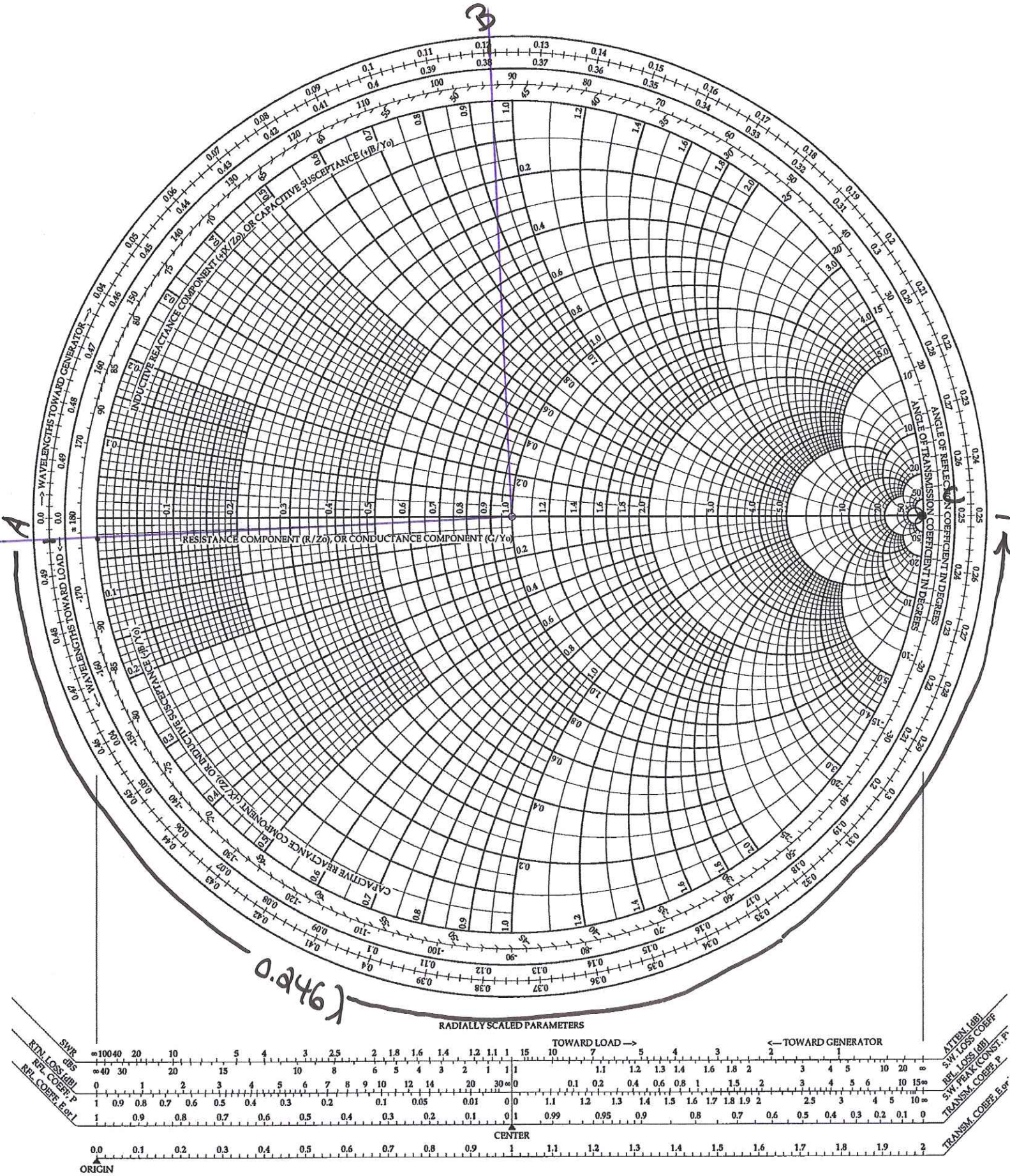



2-42

The Smith Chart

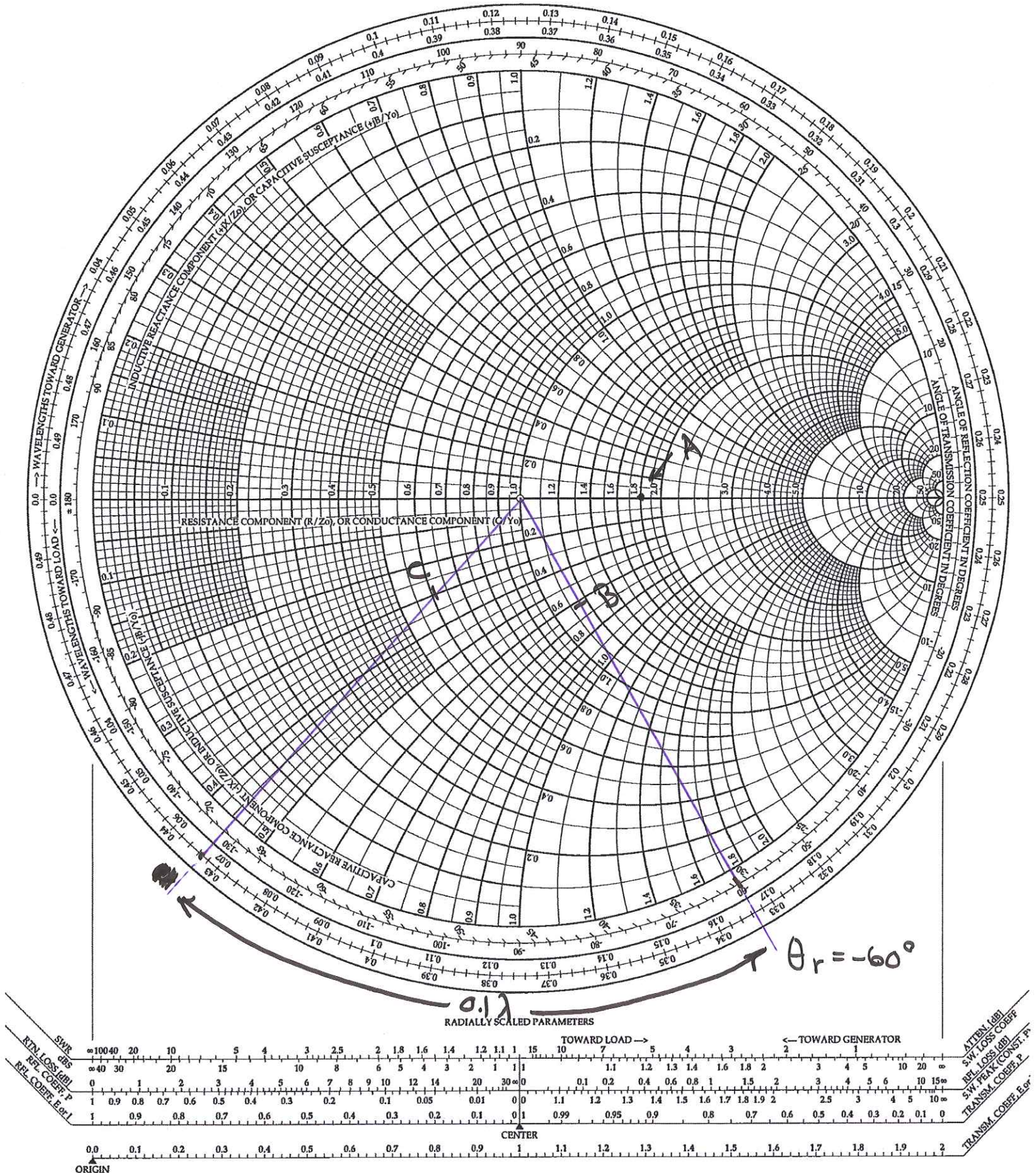


2-45
1

The Smith Chart

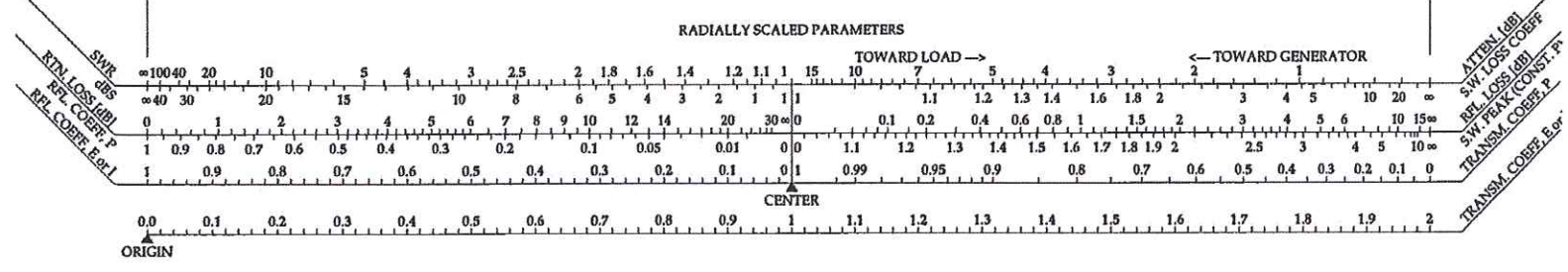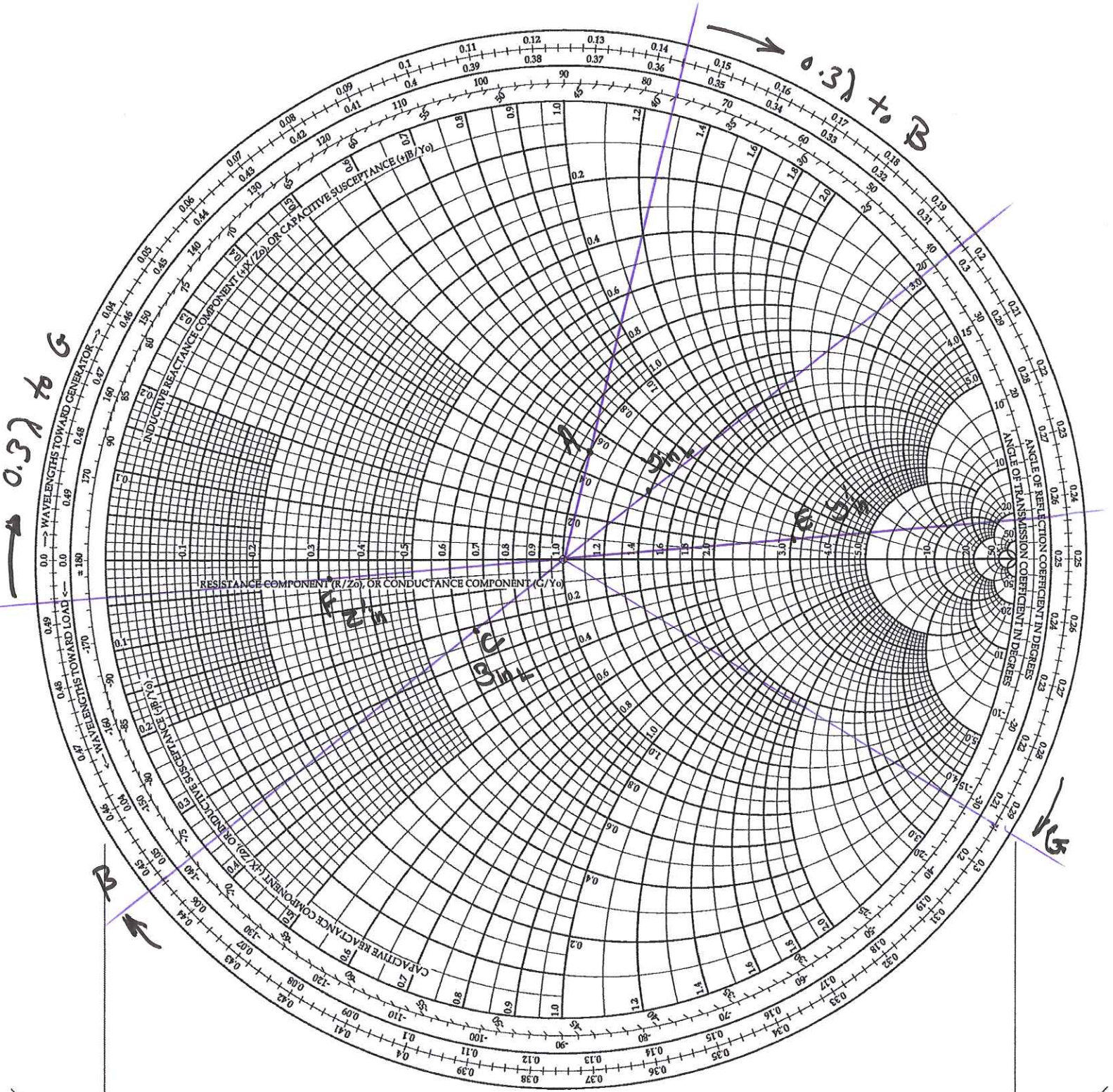

2-46
11/1

The Smith Chart

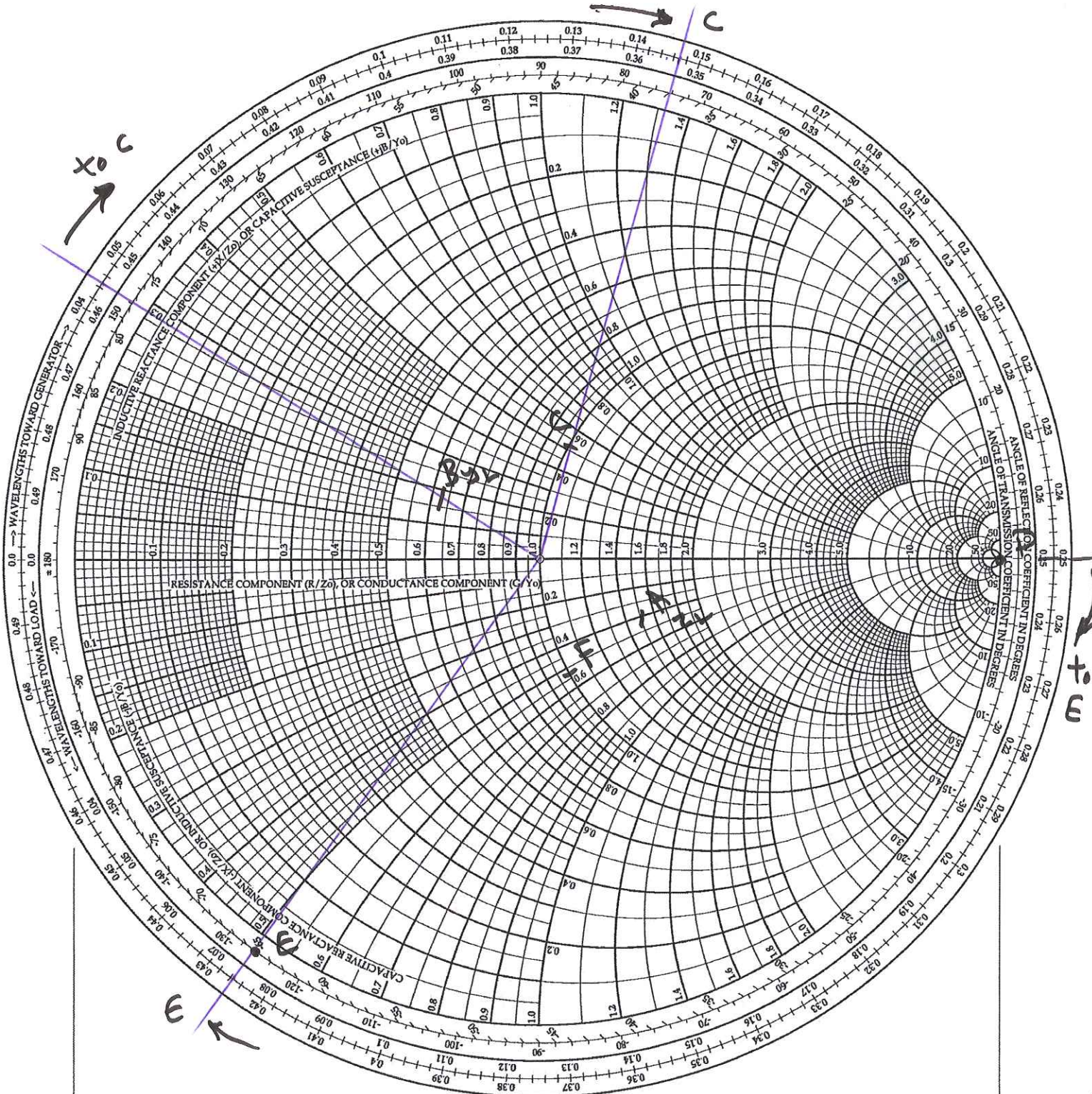

RADIALLY SCALED PARAMETERS

